

MARCH 2014						
	T	W	T	F	S	S
4	5	6	7	8	1	2
11	12	13	14	15	16	17
18	19	20	21	22	23	24
25	26	27	28	29	30	31

Basic concepts of Current Electricity

Electricity :-

It is a fundamental form of energy resulting from the presence & motion of electric charges, typically electrons, which creates an electric current. It is a form of energy that can be stored, transmitted through conductors like copper wires and converted into other form of energy, such as heat, light and motion.

Modern Electron Theory :-

In the past, to define electricity, several theories about electricity were developed through experiments & by observing its behaviour. However, the only theory that has survived is

Modern Electron Theory of Matter.

Important Notes

This theory says that every matter (whether solid, liquid or gas) consists of very small divisible particles called Molecules.

18 FEBRUARY
TUESDAY



FEBRUARY 2014						
M	T	W	T	F	S	S
3	4	5	6	7	1	2
10	11	12	13	14	8	9
17	18	19	20	21	15	16
24	25	26	27	28	22	23

A molecule is further made up of very minute particles called Atoms.

Atom has two main parts :-


→ Nucleus

→ Extra Nucleus

→ Nucleus : The central part of an atom which contains protons and neutrons is called nucleus.

→ Proton has positive charge


→ Neutron has no charge.

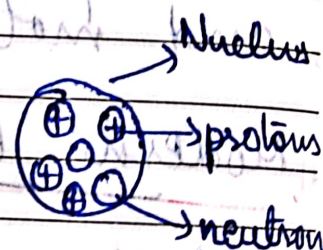

The mass of proton is equal to the mass of neutron & this total mass constitutes the entire mass of an atom.


→ Extra Nucleus : - The outer part which contains only electrons is called extra-nucleus. An e^- has negative charge (1.602×10^{-19} coulombs) equal to that of a proton. The mass of e^- is nearly $1/1840$

MARCH 2014						
S	F	T	W	T	F	S
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30					

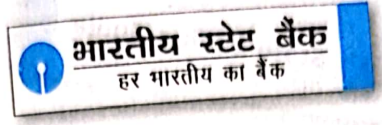

times that of a proton is usually neglected. Thus, the entire mass of an atom is constituted by the nucleus of an atom.

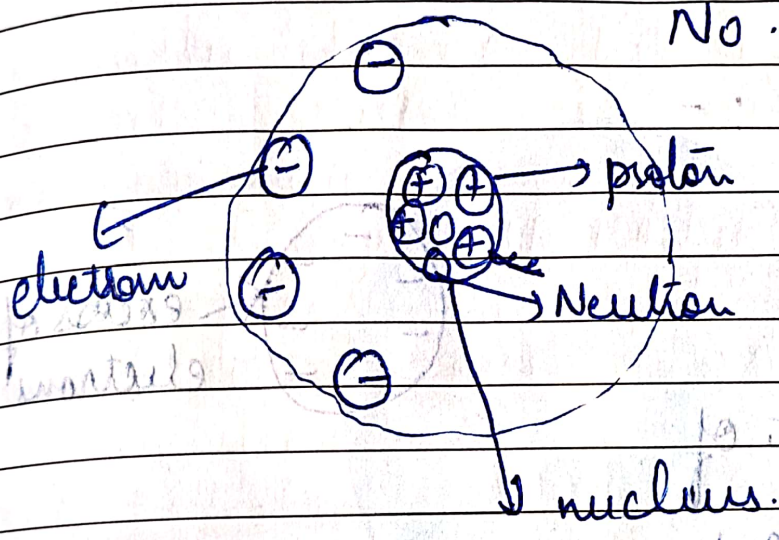Atomic weight = No. of proton + No. of neutron.



Nature of Electricity :-

- (1) A body is neutral as it has same number of protons as that of electrons.
- (2) If some of the electrons are removed from the body, there occurs a deficit

Important Notes

of electrons and the body attains a +ve charge.




FEBRUARY 2014						
M	T	W	T	F	S	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

20 FEBRUARY THURSDAY

(3) If some of the electrons are supplied to the body, there occurs excess of electrons and the body attains a -ve charge.

Charged Body :-

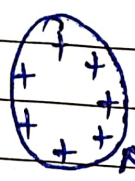

Deficit of electrons



excess of electrons

Thus a body is said to be charged positively or negatively if it has deficit or excess of electrons from its normal due to sharing respectively.

Important Notes

UNIT OF CHARGE :-

The charge of an e^- is very small but is not convenient to take it as the unit of charge.

MARCH 2014						
M	T	W	T	F	S	S
31					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30



FEBRUARY
FRIDAY
21

Therefore, "Coulomb" is used as unit of charge.

Hence, 1 Coulomb = charge of $628 \times 10^{16} e^-$.

If a body is said to have a -ve charge of one coulomb, it means that the body has an excess of 628×10^{16} electrons from its normal due share.

Free electrons :- The valence e^- which are very loosely attached to the nucleus of an atom & can be easily detached are called free electrons.

FIELDS OF CHARGES :-

Important Notes

1) Electric field :- It is force field created by electric charges, influencing other charges with a force that depends on the charge & the distance from the source.

FEBRUARY 2014						
M	T	W	T	F	S	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

1) Electric field :- "demonstrated" \rightarrow $E = \frac{F}{q}$

9 | Source :- Stationary or moving electric charges.

11 | Effect :- Exerts a force on other electric charges.

12 | Field lines :- Originate from positive charges and terminate on negative charges, forming open-ended lines.

3 | Unit :- Volts per meter

4 | Nature :- Can be attractive or repulsive.

2) Magnetic field :-

A magnetic field is created by moving charges (like electric current) or magnets.

exerting a force on other moving charges or magnetic objects.

Important Notes

MARCH 2014						
M	T	W	T	F	S	S
31					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

Source :- Moving electric charges & magnetic sources.

Effect :- Exerts a force on moving charges and other magnetic objects.

Field lines :- Emerge from the north pole & enter the south pole, forming closed loops, as there are no magnetic monopoles.


Unit :- Tesla (T)

Nature :- Can be attractive or repulsive.


The key difference between two fields are source (electric charges for electric field and moving charges for magnetic field), nature of the field lines (open^{ended} for electric field & closed loops for magnetic).



FEBRUARY 2014						
M	T	W	T	F	S	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

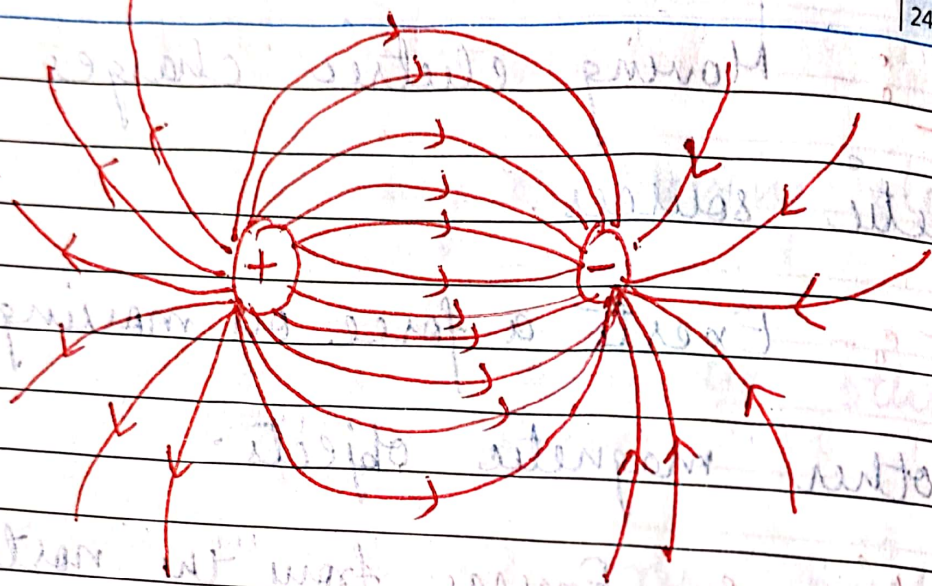

Electric fields

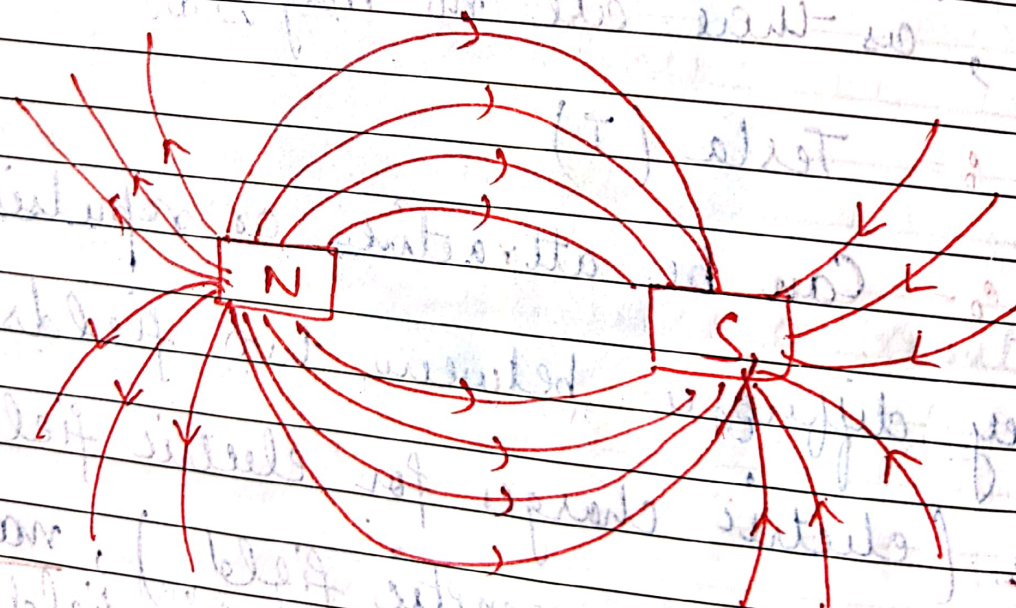

Magnetic field

Important Notes

MARCH 2014						
M	T	W	T	F	S	S
31	4	5	6	7	8	9
3	11	12	13	14	15	16
10	18	19	20	21	22	23
17	25	26	27	28	29	30
24						

Electric Potential:

When a body is charged, either electrons are supplied to it or they are removed from it. In both the cases work is done.

This work done is stored in the form of electric potential.

The capacity of a charged body to do work is called **ELECTRIC POTENTIAL**.

The measure of electric potential is the work done to charge a body to one coulomb i.e.

electric potential = $\frac{\text{work done}}{\text{charge}}$

Important Notes

$$V = \frac{W}{Q}$$

If $w = 1$ joules ; $Q = 1$ coulomb

$$V = \frac{W}{Q} = 1 \text{ volt}$$

Hence, a body is said to have an

electric potential of 1 volt if one joule of work is done to charge the body to

one coulomb.

Potential Difference :-


When a body is charged to a different electric potential as compared to the

other charged body, the two bodies are


said to have a potential difference.

Thus, the difference in the electric potential of the two charged bodies is called potential difference.

MARCH 2014						
T	W	T	F	S	S	
				1	2	
4	5	6	7	8	9	
11	12	13	14	15	16	
18	19	20	21	22	23	
25	26	27	28	29	30	

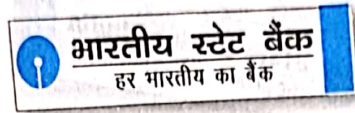

Unit :- Volt

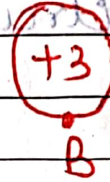


Potential difference = $+5V - +3V$

Difference between two potential (A & B) = $+2V$

CURRENT :-

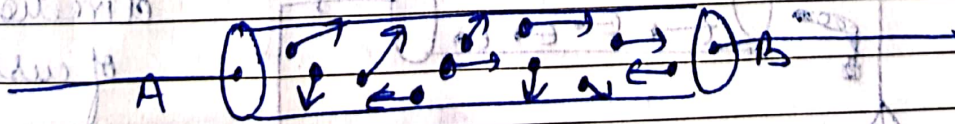In metals, a large number of free electrons are available which move from one atom to the other at random.



When a electric potential, is applied across

Important Notes


the conductor, the loosely attached free e^- starts moving towards the free terminal of the battery.

Thus, a continuous flow of electrons in an electric circuit is called electric current.

In other words, current is the flow of electrically charged particles, usually electrons, through a conductor. This flow is driven by a voltage.

Unit :- Amperes (A)

Conventional direction of current :-

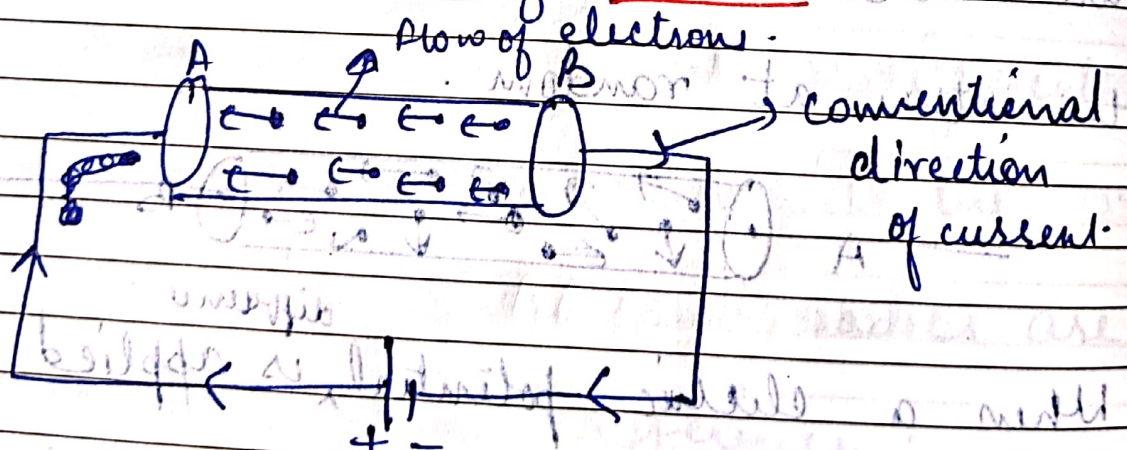

Important Notes

Mathematically

$$I = \frac{Q}{t}$$

If $Q = 1 \text{ coulomb}$
 $t = 1 \text{ sec}$

then, $I = 1 \text{ A}$


01 MARCH SATURDAY

or
$$I = \frac{dQ}{dt}$$

AC current :-

The flow of electric charge in a periodically reverse direction is called alternating current (AC). It is also referred as (AC current).


One type of alternating current may be sinusoidal.

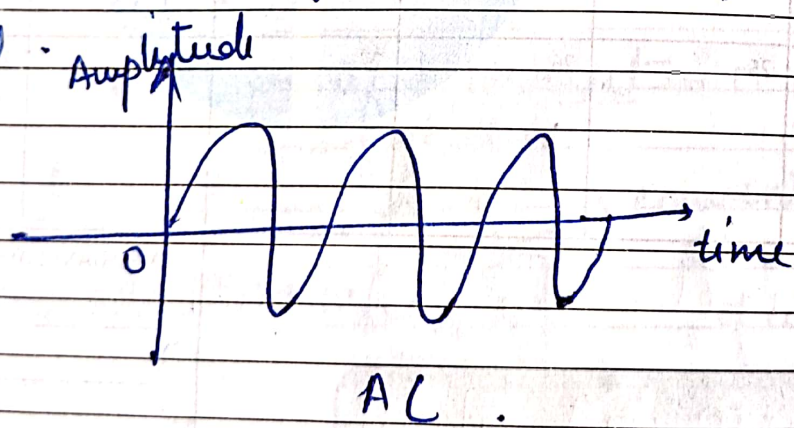


SUNDAY 02

Important Notes DC current :-

Direct current flows in one direction.

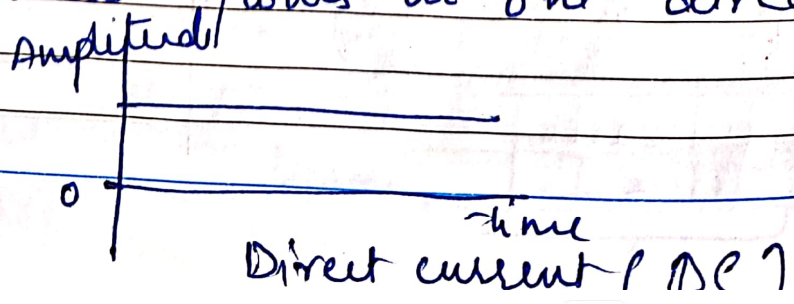

APRIL 2014						
M	T	W	T	F	S	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

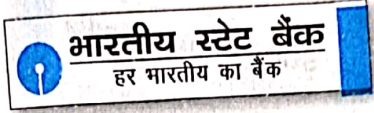

MARCH
MONDAY

03

Resistance :-

Resistance is the oppose to the flow of current (electrons)

or

The opposition offered to the flow of current is called resistance.

Unit :- It is denoted by Ω or $K\Omega$.

A wire is said to have a resistance of one ohm, if one ampere of current passing through it produces a heat of 0.24 calories

Resistivity :- (Law of Resistance)

(1) It is directly proportional to its length.
i.e $R \propto l$

Important Notes

(2) It is inversely proportional to its area of cross-section.
i.e $R \propto \frac{1}{A}$

04 MARCH
 TUESDAY

(3) It depends upon the nature of the material of which the wire is made of.

(4) It also depends upon the temperature of the wire.

Therefore

$$R \propto \frac{l}{a}$$

or

$$R = \rho \frac{l}{a}$$

where ρ is a constant of proportionality.

Called Resistivity.

OHM'S LAW :-

Whenever a potential difference (V) is applied across a conductor (or circuit),

Important Notes

some current (I) flows through it. The flow of current is opposed by the resistance (R) of the conductor. A relationship

APRIL 2014						
M	T	W	T	F	S	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

exists between the three quantities i.e.

applied voltage, current and resistance.

This relationship was expressed first by

George Simon Ohm, a German scientist.

It is called "OHM'S LAW".

Ohm's law states that the current flowing

between any two points of conductor is


directly proportional to the potential difference

across them provided physical conditions i.e.

temperature etc. do not change.

Mathematically

$$I \propto V$$

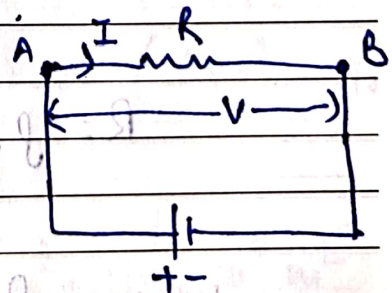

Important Notes

or $\frac{V}{I} = \text{constant}$

or $\frac{V}{I} = R$

or $V = IR$; $I = \frac{V}{R}$

MARCH 2014						
M	T	W	T	F	S	S
31						
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

Numericals

Q what should be the cross-sectional area of conductor of 1km length to transmit 200 A, so that the total voltage drop in the conductor may not exceed 12V.

The resistivity of conductor material is $3 \mu\Omega/\text{cm}^3$.

Solution:- Acc. to ohm's law.

$$\text{Resistance, } R = \frac{V}{I} = \frac{12}{200} = 0.06 \Omega$$


$$R = \rho \frac{l}{a} \quad \text{or} \quad a = \rho \frac{l}{R}$$

where $\rho = 3 \times 10^{-6} \Omega \text{ cm} = 3 \times 10^{-8} \Omega \text{ m}$

$$l = 1 \text{ km} = 1000 \text{ m}$$

$$a = \frac{3 \times 10^{-8} \times 1000}{0.06} = 5 \times 10^{-4} \text{ m}^2$$

$$= 5 \text{ cm}^2 \text{ (Ans)}$$

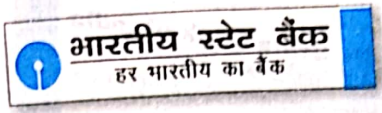

APRIL 2014						
L	M	T	W	T	F	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

A piece of 10cm^3 of copper having specific resistance of $1.7 \times 10^{-6} \Omega \text{cm}$ is

- (1) drawn into wire of 200cm length.
- (2) rolled into a square plate of 10cm side.

Determine the resistance of the wire & resistance between the opposite faces of the plates.

Solution :- $R = \rho \frac{l}{a}$ where $\rho = 1.7 \times 10^{-6} \times 10^{-2} \Omega \text{m}$

(1) Since, volume = $10 \text{cm}^3 = 10 \times 10^{-6} \text{m}^3$

Area $a = \frac{\text{Volume}}{\text{length}} = \frac{10 \times 10^{-6}}{200} = 5 \times 10^{-8} \text{m}^2$

$\therefore R = \frac{1.7 \times 10^{-8} \times 200}{5 \times 10^{-8}} = 68 \Omega$ (Ans)

(2) Area of plate = $10 \times 10 = 100 \text{cm}^2 = 100 \times 10^{-4} \text{m}^2$

length or thickness of plate = $\frac{\text{Volume}}{\text{Area}} = \frac{10 \times 10^{-6}}{100 \times 10^{-4}}$

$W = 10 \times 10^{-4} \text{m}$



M	T	W	T	F	S	S
31						
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

$$R = \frac{1.7 \times 10^8 \times 10 \times 10^{-4}}{100 \times 10^{-4}} = 0.17 \times 10^{-8}$$

$$= 0.0017 \mu\Omega$$

Energy :-

The total amount of work done in an electrical circuit is called electrical energy.

A work is said to be done by the moving stream of electrons or charge is called Electrical energy.

So,

$$V = \frac{\text{work done}}{Q}$$

Therefore work done or electrical energy's

$$W = VQ = VIt \quad (\text{since } Q = It)$$

$$W = I^2 R t$$

in terms of current

Important Notes

APRIL 2014						
M	T	W	T	F	S	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

or $W = \frac{V^2 t}{R}$ in terms of voltage.

Unit :- Joule. work done by current

If 1 volt, $I = 1$ ampere, and $t = 1$ sec
then electrical energy = 1 joule.

Electrical Power :-

The rate at which work is being done in an electrical circuit is called electrical Power.

Electrical Power = $\frac{\text{Work done in an electrical circuit}}{\text{time}}$

$$P = \frac{VIt}{t} = VI = I^2R = \frac{V^2}{R}$$

Important Notes

Unit :- Watt.

If $V = 1$ volts & $I = 1$ ampere then,
 $P = 1$ watt.



MARCH 2014						
S	M	T	W	T	F	S
31						
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

11 MARCH TUESDAY

Mechanical Power :-

The rate of doing work or the amount of work done per unit time is called power.

$Power = \frac{Work\ done}{Time}$

Unit :- Newton meters per second or joules/sec

Important Notes

$$= \frac{Nm}{s} \quad \text{or} \quad (J/s)$$



* Heat energy

~~In form of energy~~

Electrical circuits elements (R, L & C).

In electrical circuits R, L & C represents resistor, inductor & capacitor resp.

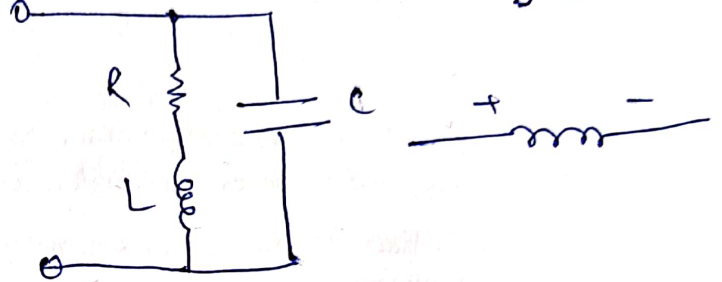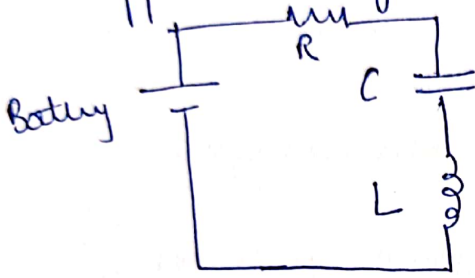- Resistor opposes current flow (measured in Ω) convert electrical energy into heat
- Inductor stores energy in a magnetic field (measured in henry (H)) opposes changes in current flow
- Capacitor stores energy in an electric field, (measured in faraday (F)) opposes changes in voltage



voltage & current source :-

voltage source - e.g (batteries)


A voltage source is a device which provides a constt voltage to load at any instance of time & is independent of the current drawn from it. This type of source is known as ideal voltage source.

It is denoted by





voltage source symbol

Ideal voltage source . Not possible .

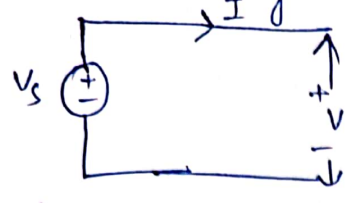

practical voltage source have some amount of internal resistance an known as practical voltage source .

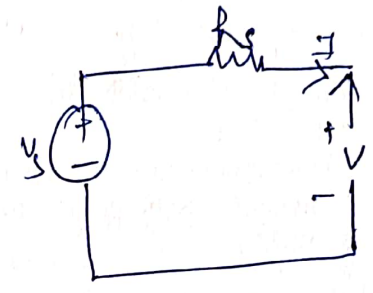
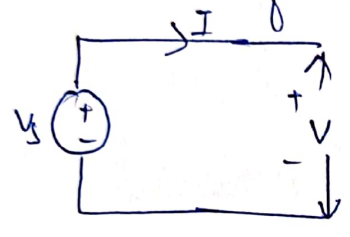
A practical voltage source is thus denoted by a resistance in series which represents the internal resistance of source .



Current source :- (e.g) solar cells, transistors


Ideal current source .

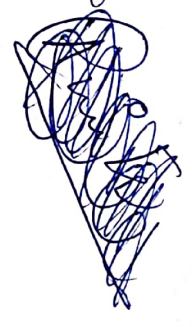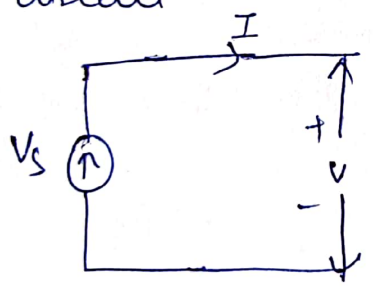A current source is a device which provides the constant current to load at any time & is independent of the voltage supplied to the circuit .



Practical current source :-

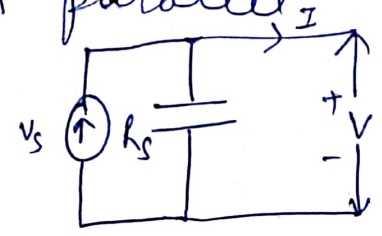
A practical current source is represented as an ideal current source connected with resistance in parallel .



Source Conversion:-

(15)

for If we have . 8Ω

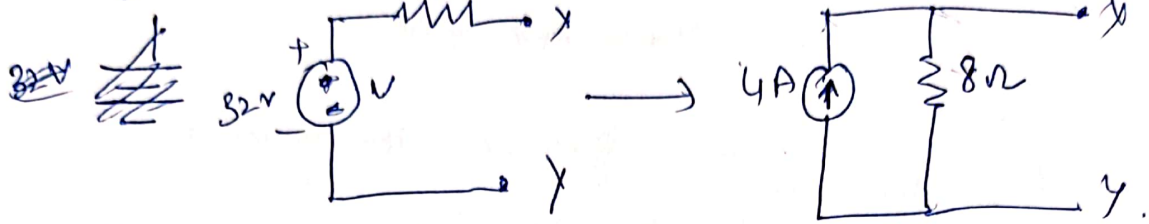

By using ohm's law .

$$V = IR$$

$$\frac{32}{8} = I = 4A.$$

A technique used in circuit analysis to simplify complex circuits by converting a voltage source in series with a resistor into an equivalent current source in parallel with the same resistor & vice-versa.

→ This conversion helps in simplifying circuit analysis

Voltage source to current source:-

A voltage source (V) in series with a resistor (R) can be transformed into a current source (I) in parallel with same resistor where $I = \frac{V}{R}$

Current source to voltage source:-

A current source (I) in parallel with a resistor (R) can be transformed into a voltage source (V) in series with same resistor where $V = I \cdot R$

DC circuits:-
Series & parallel circuits:-

Series Circuits:-

The circuit in which no. of resistors are connected end to end so that same current flows through them is called series circuit. (14)

In the circuit, three resistors R_1, R_2, R_3 are connected in series across a supply voltage V volts.


The same current (I) is flowing through all 3 resistors. If V_1, V_2 & V_3 are the voltage drops across the 3 resistors R_1, R_2 & R_3 resp. then,

$$V = V_1 + V_2 + V_3 = IR_1 + IR_2 + IR_3 \quad (\text{As per Ohm's law})$$

Let R be the total resistance of the circuit, then

$$IR = IR_1 + IR_2 + IR_3 \quad \text{or} \quad R = R_1 + R_2 + R_3$$

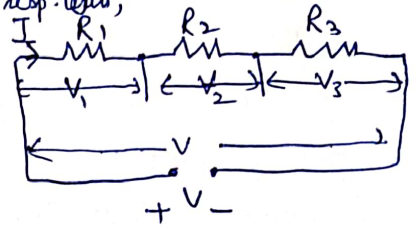i.e. Total Resistance = \sum Individual resistances.




Application:- In the circuit, all the lamps are connected by a single switch, they can't be controlled individually.

Parallel circuit:-

The circuit in which one end of all the resistors is joined to a common point & the other ends are also joined to another common point so that different current flows through them is called parallel circuit.

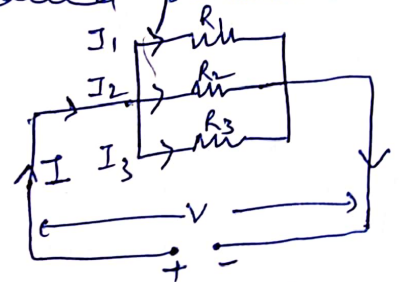Three resistors R_1, R_2 & R_3 are connected in parallel across voltage V . Current flowing through them is I_1, I_2 & I_3



Total current is

$$I = I_1 + I_2 + I_3 = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \quad (\text{Ohm's law})$$

Let R is the total resistance or effective, then


$$\frac{V}{R} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \quad \text{or} \quad \frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Reciprocal of total resistance = sum of reciprocal of individual resistances.

* Series-parallel circuit:-

Circuit in which series & parallel circuits are connected in series is called S-P circuits.

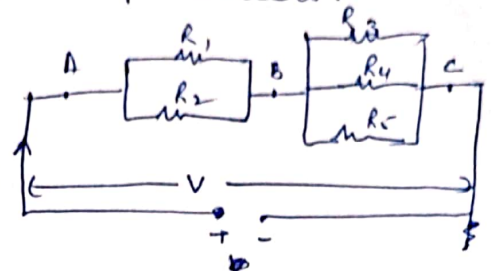- (1) Across terminal AB → R₁ & R₂ are connected in parallel.
- (2) Across BC → R₃, R₄ & R₅ are connected in parallel.
- (3) R_{AB} & R_{BC} are connected in series with each other.



Total or effective resistance of the circuit is :-

$$\frac{1}{R_{AB}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2} \quad \text{or} \quad R_{AB} = \frac{R_1 R_2}{R_1 + R_2}$$

Similarly

$$\frac{1}{R_{BC}} = \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} = \frac{R_3 R_4 + R_4 R_5 + R_5 R_3}{R_3 R_4 R_5}$$


$$\text{or} \quad R_{BC} = \frac{R_3 R_4 R_5}{R_3 R_4 + R_4 R_5 + R_5 R_3}$$

Total resistance of the circuit is $R = R_{AB} + R_{BC}$

* Division of current in parallel circuit.

when two resistors are connected in parallel.

Acc. to Ohm's law

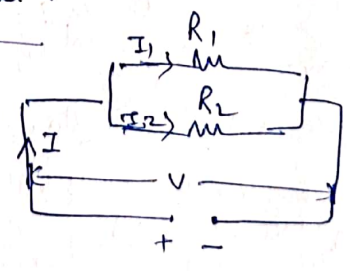

$$I_1 R_1 = I_2 R_2 = IR = V \quad \text{or} \quad \frac{I_1}{I_2} = \frac{R_2}{R_1}$$

The value of branch current can also be expressed in terms of total circuit current.

$$I_1 R_1 = I_2 R_2 = IR = V \quad \text{where } I \text{ \& } R \text{ are the total resistance \& current}$$

$$R = \frac{R_1 R_2}{R_1 + R_2}$$

$$\text{Now } I_1 R_1 = IR = I \frac{R_1 R_2}{R_1 + R_2} \quad \text{or} \quad I_1 = \frac{I R_1 R_2}{R_1 (R_1 + R_2)} = \frac{I R_2}{R_1 + R_2}$$

$$\text{Similarly } I_2 R_2 = IR = I \frac{R_1 R_2}{R_1 + R_2} \quad \text{or} \quad I_2 = \frac{I R_1 R_2}{R_2 (R_1 + R_2)} = \frac{I R_1}{R_1 + R_2}$$

APRIL 2014						
M	T	W	T	F	S	S
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

Series & Parallel Circuits

Q A 100W, 250V bulb is put in series with a 40W, 250V bulb across 500V supply. What will be the current

consumed by each bulb & will such a combination work?

Solution:-

Resistance of 100W bulb

$$R_1 = \frac{V^2}{W_1} = \frac{(250)^2}{100} = 625 \Omega$$


Resistance of 40W bulb

$$R_2 = \frac{V^2}{W_2} = \frac{(250)^2}{40} = 1562.5 \Omega$$


These resistances are connected in series

Important Notes
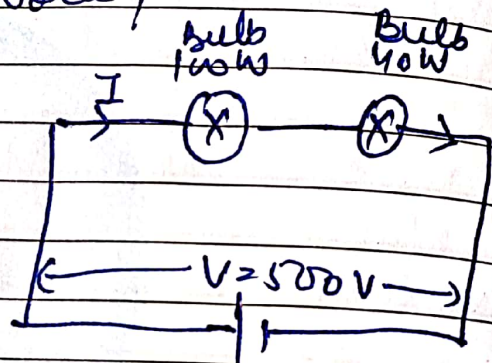
$$\begin{aligned} \text{Total } R &= R_1 + R_2 = 625 + 1562.5 \Omega \\ &= 2187.5 \Omega \end{aligned}$$



MAY 2014						
S	T	W	T	F	S	S
			1	2	3	4
5	6	7	8	9	10	11
2	13	14	15	16	17	18
9	20	21	22	23	24	25
6	27	28	29	30	31	

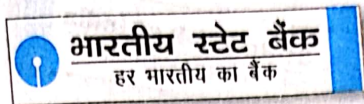

Current drawn from 500V supply $I = \frac{V}{R}$

$$= \frac{500}{2187.5} = 0.2286A$$

Power consumed by 100W $P_1 = I^2 R_1 = (0.2286)^2 \times 625$

$$= 32.65W$$

Power consumed by 40W $P_2 = I^2 R_2 = (0.2286)^2 \times 1562.5$

$$= 81.63W$$

This combination will not work. The reason is that when 40W bulb will draw a power of 81.63W its filament will be overheated & will burn.

Q A resistor R is connected in series with a parallel circuit comprising of two resistances 12Ω & 8Ω resp.

Important Notes

The total power dissipated in the circuit is 96 watts when applied voltage is 24V. Calculate the value of R .




MTWTFSS	APRIL 2024
7	1 2 3 4
14	8 9 10 11
21	15 16 17 18
28	22 23 24 25
	29 30

12

APRIL
SATURDAY

Sol:- Total dissipated power = 96 W

Applied voltage = 24 V

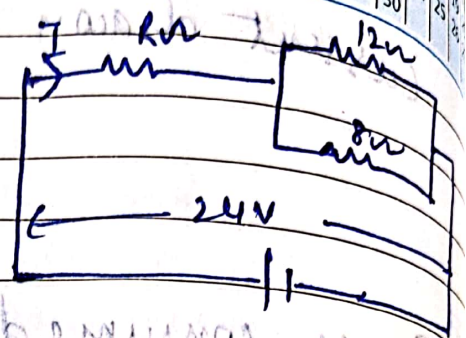

Equivalent resistance of the two resistances connected in parallel say R_p .

$$\frac{1}{R_p} = \frac{1}{12} + \frac{1}{8}$$

$$= \frac{2+3}{24} = \frac{5}{24}$$

$$R_p = \frac{24}{5} = 4.8 \Omega$$

Current supplied to the circuit,

$$I = \frac{P}{V} = \frac{96}{24} = 4 A$$

Effective resistance of the circuit $R_{eff} = \frac{V}{I} = \frac{24}{4} = 6 \Omega$

Important Notes

$R_{eff} = R + R_p$

$$R = R_{eff} - R_p = 6 - 4.8 = 1.2 \Omega$$


6	7	8
13	14	15
20	21	22
27	28	29

APRIL 2014						
T	W	T	F	S	S	
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

Network Terminology

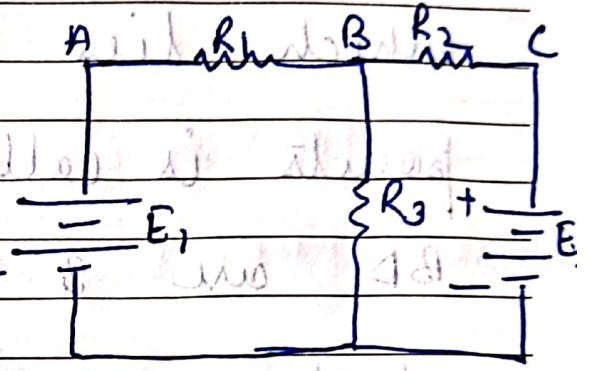1. Active Element :-

The element which supplies energy to the circuit is called active element. E_1 and E_2 are active elements.



2. Passive Element :- The element which

receives energy is called passive element (such as resistor, inductor and capacitor). R_1, R_2 and R_3 are passive elements.

3. Node :- It is a point in the network where ~~three~~ ^{two} or more circuit elements are joined. ~~It is a point where~~ ~~connected in circuit~~. A, B, C and D are nodes

4. Junction :- It is a point in the network where three or more circuit elements are joined. It is point where current is

divided. B & D are the junctions.

5. Branch :- The part of network which lies between two junction points is called branch. DAB, BCD & BD are 3 branches.

6. Loop :- The closed path of a network is called loop. ABDA, BCDB & ABCDA are 3 loops.

7. Mesh :- The most elementary form of a loop which cannot be further divided is called Mesh. ABDA & BCDB are 2 Mesh.

Important Notes

28

APRIL 2014

	S	M	T	W	T	F	S	S
							5	6
7	8	9	10	11	12	13		
14	15	16	17	18	19	20		
21	22	23	24	25	26	27		
28	29	30						

KIRCHHOFF'S LAWS

$$\sum I = 0$$

KVL

KCL

Kirchoff voltage law Kirchoff Current Law.

Kirchoff 1st law :-


It is also known as Kirchoff's Current Law (KCL).

It states that :-

The algebraic sum of all the currents meeting at a point or junction is zero.

Mathematically, $\sum I = 0$

Algebraic sum is to be taken,

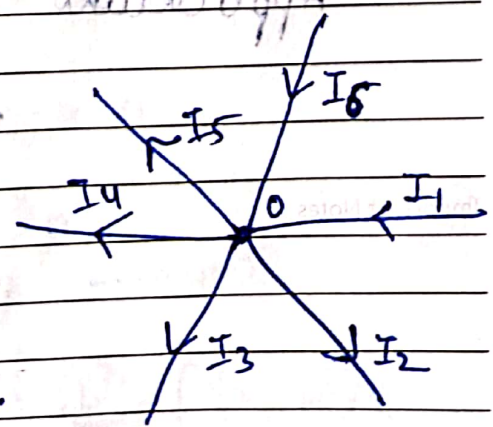

consider.

Incoming currents as +ve.

Outgoing currents as -ve.



MARCH 2014						
M	T	W	T	F	S	S
31						
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

15

MARCH SATURDAY

Applying KCL to junction O.

$$I_1 - I_2 - I_3 - I_4 - I_5 + I_6 = 0$$

$$I_1 + I_6 = I_2 + I_3 + I_4 + I_5$$

Application - Nodal Analysis

Kirchhoff's Second Law :- follow path

In a closed circuit or Mesh, the algebraic sum of all the e.m.f.'s plus the algebraic sum of all the voltage drops (product of current & resistance) is zero.

$$\sum E + \sum V = 0$$

Application → Loop Analysis

→ Mesh Analysis.

SUNDAY 16

Important Notes


APRIL 2014						
M	T	W	T	F	S	S
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

Numericals of KVL

OPES (Loop Analysis)


Q1 In the circuit, calculate current and power in the 6Ω resistor?

Sol: Apply KVL to loop

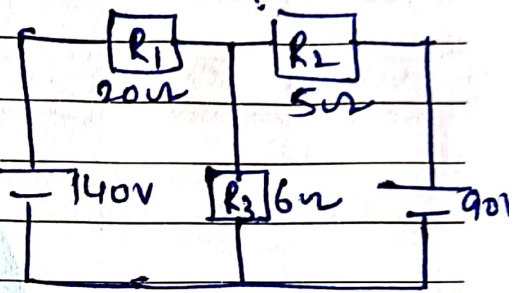

Define directions of current.

Apply KVL to loop ABEFA we get.

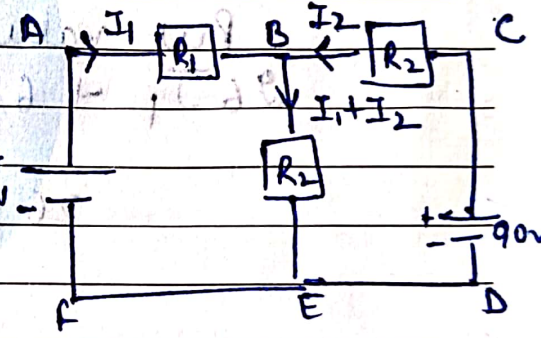

$$20I_1 + 6(I_1 + I_2) - 140 = 0$$

$$26I_1 + 6I_2 = 140 \quad \text{--- (1)}$$

Apply KVL to loop BCDEBC.

$$5I_2 + 6(I_1 + I_2) - 90 = 0$$

Important Notes

$$5I_2 + 6I_1 + 6I_2 = 90$$

$$6I_1 + 11I_2 = 90 \quad \text{--- (2)}$$

Solving eq (1) & (2) (for like terms)

$$6(26I_1 + 6I_2 = 140) \quad \text{Multiply eq (1) by 6}$$

$$26(6I_1 + 11I_2 = 90) \quad \text{Multiply eq (2) by 26}$$



MARCH 2014						
S	M	T	W	T	F	S
31						
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

18 MARCH TUESDAY

1156 I₁ + 36 I₂ = 1840

156 I₁ + 1286 I₂ = 2340

+ 250 I₂ = +1500

I₂ = 1500 / 250

I₂ = 6

Put value of I₂ in eq (1)

26 I₁ + 6(6) = 140

26 I₁ = 140 - 36

I₁ = 104 / 26

I₁ = 4

I₁ = 4

Important Notes

Current across 6 ohm = I₁ + I₂ = 4 + 6 = 10 A

Now power across 6 ohm is :-

power in 6 ohm resistor = I² R₃

(10)² = I₁² + I₂²


(10)² = (4)² + I₂²

APRIL 2014						
M	T	W	T	F	S	S
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

$$P = 600 \text{ W}$$

Q Using Kirchhoff's law, solve the n/w shown & find the current in each branch.

Sol:- First make current direction

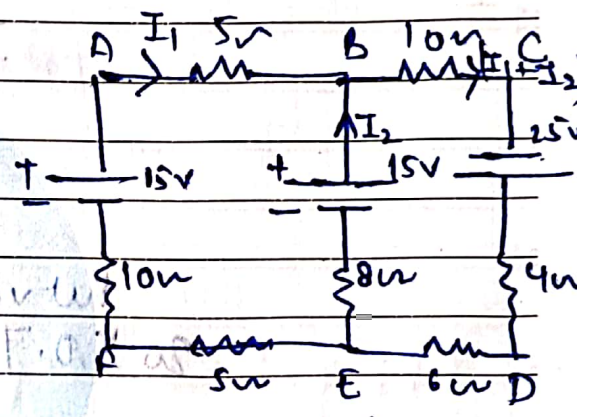

Apply KVL to loop AB EFA

$$5I_1 + 10I_1 + 8I_2 + 5I_1 + 10I_1 - 15 = 0$$

$$20I_1 + 8I_2 = 0 \quad \text{--- (1)}$$

$$I_1 = 0.4I_2 \quad \text{--- (2)}$$

$5I_1 = 0$
 $10I_1 = 40$
 $10(I_1 + I_2) - 25 + 4(I_1 + I_2) + 6I_2 + 8I_2 + 6I_1 - 15 = 0$
 $20I_1 + 10I_2 + 4I_1 + 4I_2 + 6I_2 + 8I_2 + 6I_1 = 40$

$$10(I_1 + I_2) - 25 + 4(I_1 + I_2) + 6I_2 + 8I_2 + 6I_1 - 15 = 0$$

$$20I_1 + 10I_2 + 4I_1 + 4I_2 + 6I_2 + 8I_2 + 6I_1 = 40$$

Important Notes

$$20I_1 + 28I_2 = 40 \quad \text{--- (3)}$$

Again solve eq (1) & eq (2) by like terms.

$$\begin{cases} 20I_1 + 8I_2 = 0 \\ 20I_1 + 28I_2 = 40 \end{cases}$$

APRIL 2014						
S	M	T	W	T	F	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

By putting the value of I_1 from

eq (2) to eq (3) we get

we get,

$$20(0.4I_2) + 28I_2 = 40$$

$$8I_2 + 28I_2 = 40$$

$$36I_2 = 40$$

$$I_2 = \frac{40}{36}$$

$$I_2 = 1.11 \text{ A}$$

Now put value of I_2 in eq (2) so, $I_1 = 0.4 \times 1.11 = 0.44 \text{ A}$

put I_1, I_2 values $I_1 + I_2 = 0$

$$0.44 + 1.11 = 1.55 \text{ A}$$

$$I_1 + I_2 = 1.55 \text{ A}$$

Important Notes


$$OP = 25.0 \text{ A}$$

$$OP = 25.0 \text{ A}$$

MARCH 2014						
S	M	T	W	T	F	S
31						
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

Q. Solve the circuit for the current through $6\ \Omega$ resistor.

Sol: - First make current directions

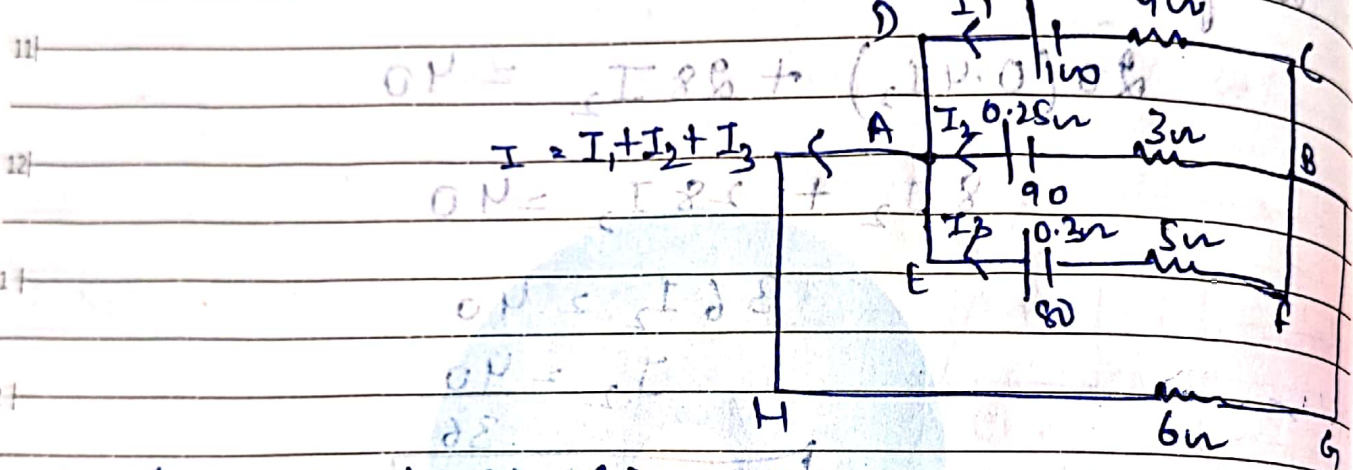

Apply KVL loop CDAHGBC

$$6(I_1 + I_2 + I_3) + 4I_1 + 0.25I_1 - 100 = 0 \text{ (KVL loop)}$$

$$6I_1 + 6I_2 + 6I_3 + 4I_1 + 0.25I_1 = 100$$

$$10.25I_1 + 6I_2 + 6I_3 = 100 \quad \text{--- (1)}$$

Apply KVL loop BAHGB

$$6(I_1 + I_2 + I_3) + 3I_2 + 0.25I_2 - 90 = 0 \text{ (KVL loop)}$$

$$6I_1 + 6I_2 + 6I_3 + 3I_2 + 0.25I_2 = 90$$

$$6I_1 + 9.25I_2 + 6I_3 = 90 \quad \text{--- (2)}$$

APRIL 2014						
M	T	W	T	F	S	S
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

Apply KVL to loop FEAHGDF

$$6(I_1 + I_2 + I_3) + 5I_3 + 0.3I_3 - 80 = 0$$

$$6I_1 + 6I_2 + 6I_3 + 5I_3 + 0.3I_3 = 80$$

$$6I_1 + 6I_2 + 11.3I_3 = 80 \quad \text{--- (2)}$$

Subtract eq (2) from (1)

$$4.2I_1 - 3.25I_2 = 10 \quad \text{--- (4)}$$

Solve (2) & (3)

$$31.08I_1 + 68.525I_2 = 5137 \quad \text{--- (5)}$$

From eq (4) & (5) we get

$$391.15I_2 = 1937.4$$

$$I_2 = \frac{1937.4}{391.15} = 4.953 \text{ A}$$

Solving eq (5) we get (put value of I_2)

$$I_1 = 2.621 \text{ A}$$

Solving eq (3) we get (putting value of I_1 & I_2)

$$I_3 = 1.15 \text{ A}$$

Important Notes



M	T	W	T	F	S	S
31						
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30


25 MARCH TUESDAY

Current in 6Ω resistor = $I_1 + I_2 + I_3$
 $= 6.21 + 4.95 + 1.15$

$$I = 12.313A$$

Q By using KVL, find the current in XY in the circuit.

Sol: First make direction of current

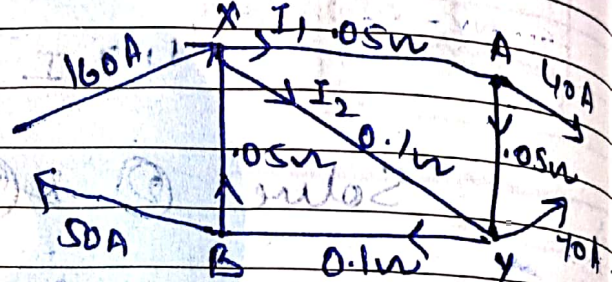

Apply KVL, loop XYAX

$$0.05I_1 + 0.5(I_1 - 40) - 0.1I_2 = 0$$

$$1.05I_1 + 0.5I_1 - 0.1I_2 = 20$$

$$1.55I_1 - I_2 = 20 \quad \text{--- (1)}$$

Apply KVL, loop XYBX

$$0.1I_2 + 0.1(I_1 + I_2 - 110)$$

$$+ 0.05(I_1 + I_2 - 160) = 0$$

$$0.1I_2 + 0.1I_1 + 0.1I_2 + 0.1I_1 + 0.05I_1 + 0.05I_2$$

$$- 8 = 0$$

At point X current is I_1

At node A. current is $I_1 - 40$

At point Y current is $I_1 - 40 + I_2 - 70$
 $I_1 + I_2 - 110$

At point B. $I_1 + I_2 - 160$

Important Notes

APRIL 2014						
M	T	W	T	F	S	S
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

$$0.15 I_1 + 0.25 I_2 = 19 \quad \text{--- (1)}$$

$$3 I_1 + 5 I_2 = 380 \quad \text{--- (2)}$$

Multiply eq (1) by 3 & subtract from eq (2) we get.

$$8 I_2 = 320$$

current in x y	$I_2 = \frac{320}{8} = 40 \text{ A}$
----------------	--------------------------------------

~~Q. For the n/w, calculate the current in the resistor~~

$$\text{--- (1) --- } a I = \dots$$

Q. For the n/w, calculate the current in the resistor

$$a I = \dots$$

Important Notes

$$42.0 = I$$

$$A = 2.0 \times 10 = 20$$




31	4	5	6	7
3	10	11	12	13
10	17	18	19	20
24	25	26	27	28

27 MARCH THURSDAY

Q Find the value of R & the current through it in the circuit shown, where the current is zero in branch OA.

Sol:- First make current direction I_1

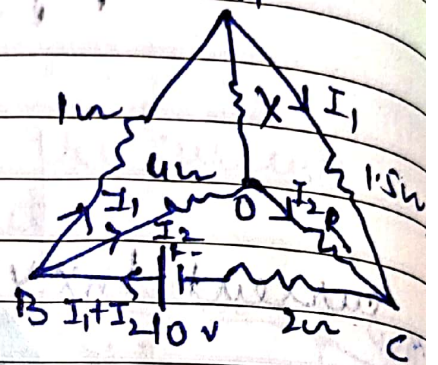

Apply KVL loop BAOB

$$I_1 - 4 I_2 = 0$$

$$I_1 = 4 I_2 \quad \text{--- (1)}$$

Apply KVL loop BAEB

$$I_1 + 1.5 I_1 + 2(I_1 + I_2) - 10 = 0$$

$$4.5 I_1 + 2 I_2 = 10 \quad \text{--- (2)}$$

Put value of I_1 from eq (1) to eq (2)

$$4.5(4 I_2) + 2 I_2 = 10$$


Important Notes

$$I_2 = 0.5 A$$

$$I_1 = 4 \times 0.5 = 2 A$$

Apply KVL to loop BOCB

APRIL 2014						
M	T	W	T	F	S	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

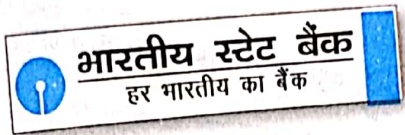


MARCH
FRIDAY

28

$$4I_1 + RI_2 + 2(I_1 + I_2) - 10 = 0$$

$$4 \times 0.5 + R \times 0.5 + 2(0.5 + 2) = 10$$

$$R = 6 \Omega$$

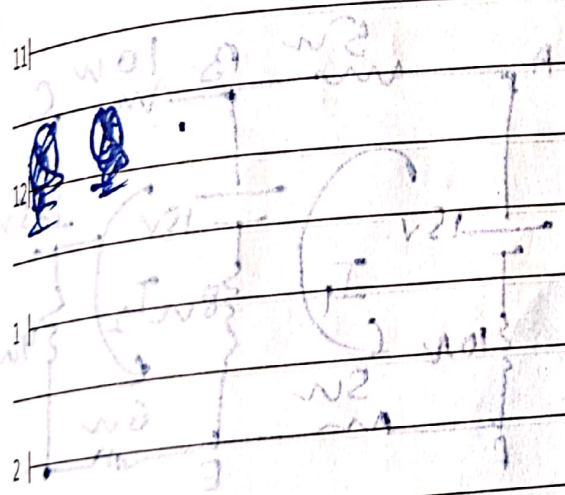

Handwritten notes and calculations, including the equation $0 = I_1 + I_2 + I_3 + I_4 + I_5 + I_6 + I_7 + I_8 + I_9 + I_{10} + I_{11} + I_{12} + I_{13} + I_{14} + I_{15} + I_{16} + I_{17} + I_{18} + I_{19} + I_{20} + I_{21} + I_{22} + I_{23} + I_{24} + I_{25} + I_{26} + I_{27} + I_{28} + I_{29} + I_{30}$.

MARCH 2014						
M	T	W	T	F	S	S
31						
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

29


MARCH
SATURDAY

KVL

Mesh Analysis

Solve the n/w shown, & find the current in each branch.

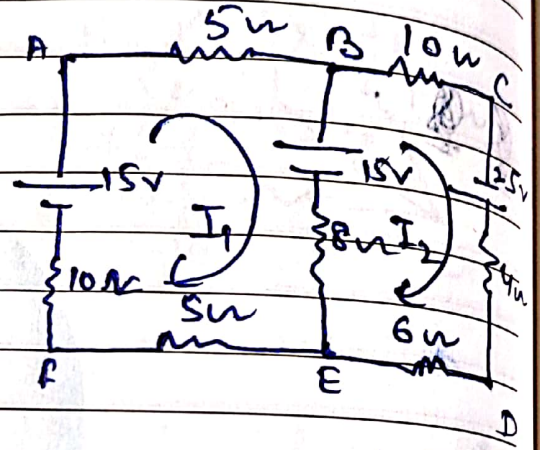Solve! - First make direction of current in two Mesh.



Apply KVL to Mesh ABEFA

$$5I_1 + 15 + 8(I_1 - I_2) + 5I_1 + 10I_1 - 15 = 0$$

$$5I_1 + 8I_1 - 8I_2 + 5I_1 + 10I_1 = 0$$

$$28I_1 - 8I_2 = 0$$

$$I_2 = 3.5 I_1 \quad \text{--- (1)}$$

Apply KVL to Mesh BCDEB

SUNDAY 30

Important Note

$$10I_2 - 25 + 4I_2 + 6I_2 + 8(I_2 - I_1) - 15 = 0$$

$$10I_2 - 40 + 4I_2 + 6I_2 + 8I_2 - 8I_1 = 0$$

$$28I_2 - 8I_1 = 40 \quad \text{--- (2)}$$

APRIL 2014						
M	T	W	T	F	S	S
7	1	2	3	4	5	6
14	8	9	10	11	12	13
21	15	16	17	18	19	20
28	22	23	24	25	26	27
29	30					

Put value of I_2 from eq (1) to eq (2)

$$(28(-3.5 I_1)) - 8 I_1 = 40$$

$$0 = (-119 I_1) - 8 I_1 = 40$$

$$-127 I_1 = 40$$

$$I_1 = \frac{40}{-127}$$

$$I_1 = 0.444 A$$

Put value of I_1 in eq (1)

$$I_2 = 3.5 \times 0.444 = 1.54 A$$

$$I_2 = 1.54 A$$


Current in branch EB = $I_1 - I_2 = -1.1 A$

$$I_1 - I_2 = 0.444 - 1.54 = -1.1 A$$

Solve the circuit shown for the current through 6 ohm resistor

Important Notes

Sol:- first make directions of current.

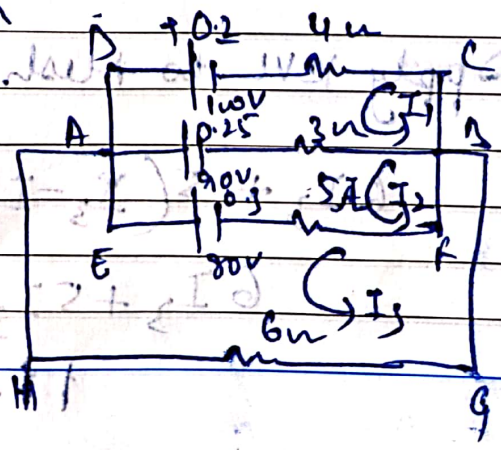



MARCH 2014						
M	T	W	T	F	S	S
31					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

Take Mesh CDAB. I_1 is current loop

$$90 + 0.25(I_1 - I_2) + 3(I_1 + I_2)$$

$$+ 4(I_1) - 100 + 0.2(I_1) = 0$$

$$0.25I_1 - 0.25I_2 + 3I_1 - 3I_2 + 4I_1$$

$$+ 0.2I_1 = 10$$

$$7.45I_1 - 3.25I_2 = 10 \quad \text{--- (1)}$$

Apply KVL to Mesh BA EFB. I_2 is current loop

$$80 + 0.3(I_2 - I_3) + 5(I_2 - I_3) + 3(I_2 - I_1)$$

$$+ 0.25(I_2 - I_1) - 90 = 0$$

$$0.3I_2 - 0.3I_3 + 5I_2 - 5I_3 + 3I_2 - 3I_1$$

$$+ 0.25I_2 - 0.25I_1 = 10$$

$$3.25I_1 + 8.55I_2 - 5.3I_3 = 10 \quad \text{--- (2)}$$

Apply KVL to Mesh FEAHGBF

$$6I_3 + 5(I_3 - I_2) + 0.3(I_3 - I_2) - 80 = 0$$

$$6I_3 + 5I_3 - 5I_2 + 0.3I_3 - 0.3I_2 = 80$$

$$11.3I_3 - 5.3I_2 = 80 \quad \text{--- (3)}$$

APRIL 2014						
MI	TU	W	TH	F	S	S
	1	2	3	4	5	6
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30				

01

APRIL
TUESDAY

Eliminating I_1 from eq (1) & (2) we get

$$16.31 I_2 - 12.15 I_3 = -32.92$$

Eliminating I_2 from eq (3) & (4) we get

$$-22.62 I_3 = 279.11$$

$$\text{or } I_3 = -12.339 \text{ A}$$

Negative sign shows that the actual flow of current in b_r is opposite

Important Notes


MAY 2014						
S	M	T	W	T	F	S
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30	31	

NODAL ANALYSIS

Q Find the magnitude & direction of the currents in all branches of the circuit using Kirchhoff's law. All resistances are in ohms.

Sol:-

First make directions of current.

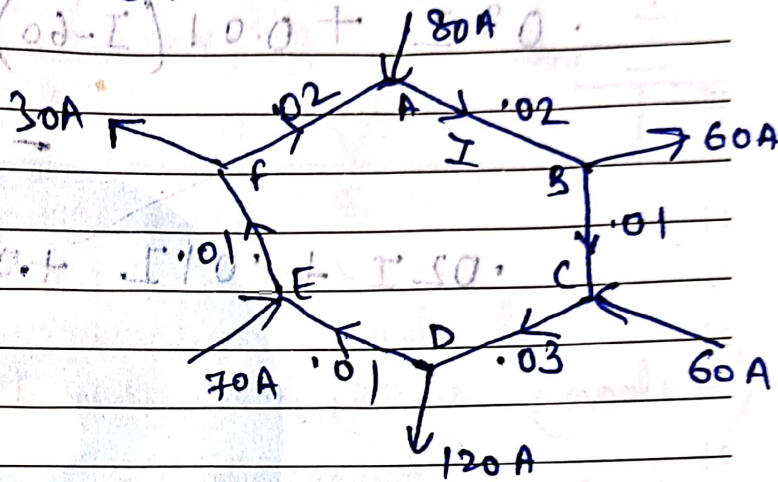

At point A assume current to be I.

At point B current is I.

(take incoming & outgoing current both)
So, $I = 60$

At point C, current is

$$I = 60 + 60 = 120$$

At point D current is

$$I = 120$$

At point E current is

$$I = 120 + 70 = 190$$

At point F current is

$$I = 190 - 30 = 160$$

Important Notes



MIT	APRIL 2014						
	1	2	3	4	5	6	7
7	8	9	10	11	12	13	14
14	15	16	17	18	19	20	21
21	22	23	24	25	26	27	28
28	29	30					

So equation will be after applying KVL

Multiply corresponding current with their resistances.

$$0.02I + 0.01(I-60) + 0.03I + 0.01(I-20) - 0.01(I-50) + 0.02(I-80) = 0$$

$$0.02I + 0.01I + 0.03I + 0.01I + 0.01I + 0.02I = 0.6 + 1.2 + 0.5 + 1.6$$

$$0.1I = 3.9$$

$$I = 39A$$

$$I_{AB} = 39A \quad (A \text{ to } B)$$

$$I_{BC} = I - 60 = -21A \quad (C \text{ to } B)$$

$$I_{CD} = I = 39A \quad (C \text{ to } D)$$

Important Notes $I_{DE} = I - 120 = -81A \quad (E \text{ to } D)$


$$I_{EF} = 0.02I + 50 = -11A \quad (F \text{ to } E)$$

$$I_{FA} = I - 80 = -41A \quad (A \text{ to } F)$$

MAY 2014						
S	T	W	T	F	S	S
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30	31	

Q For the circuit, find the current in various branches by nodal analysis.

Sol:-
for nodal cases.

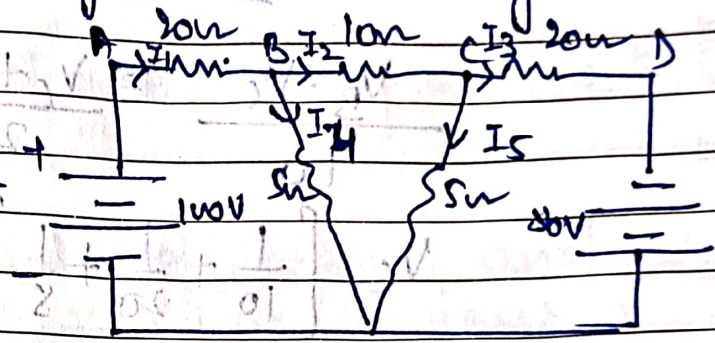

1) First find independent nodes (nodes which have 3 or more than 3 elements joined)

(A, B & C)

2) Take one node as reference node & that node is considered zero. (node E)

3) Then first make direction of current across each branch (conventional direction of current).

Solve: -

At node B

incoming current = outgoing current.

$$I_1 = I_2 + I_4$$

Source-destination

(S-D)

Important Notes

$$\frac{100 - V_B}{20} = \frac{V_B - V_C}{10} + \frac{V_B}{5}$$

$$V_B \left(\frac{1}{20} + \frac{1}{10} + \frac{1}{5} \right) - \frac{100 - V_C}{20} = 0$$

$$7V_B - 2V_C - 100 = 0 \quad \text{--- (1)}$$



	M	T	W	T	F	S	S
		1	2	3	4	5	6
7	8	9	10	11	12	13	14
14	15	16	17	18	19	20	21
21	22	23	24	25	26	27	28
28	29	30					

At node C

$$I_2 = I_3 + I_5$$

$$\frac{V_B - V_C}{10} = \frac{V_C + 50}{20} + \frac{V_C}{5}$$

$$V_C \left(\frac{1}{10} + \frac{1}{20} + \frac{1}{5} \right) - \frac{V_B + 50}{20} = 0$$

$$7V_C - 2V_B + 50 = 0 \quad \text{--- (2)}$$

From eq (1) & (2)

$$V_B = \frac{40}{3} = 13.33 \text{ V}$$

$$V_C = -\frac{10}{3} \text{ V} = -3.33 \text{ V}$$

Current in various branches

$$I_1 = \frac{100 - V_B}{20} = 2.4 \text{ A} \quad \text{from A to B}$$

$$I_2 = \frac{V_B - V_C}{10} = 1.67 \text{ A} \quad \text{from B to C}$$

$$I_3 = \frac{V_C + 50}{20} = 2.33 \text{ A} \quad \text{from C to D}$$

Important Notes

SUNDAY 06

MAY 2014						
S	M	T	W	T	F	S
5	6	7	8	9	10	11
12	13	14	15	16	17	18
19	20	21	22	23	24	25
26	27	28	29	30	31	


$$I_4 = \frac{V_B}{5} = 2.67A \quad \text{from D to E}$$

$$I_5 = \frac{V_C}{5} = -0.67A \quad \text{from E to C}$$

Q. Using method of nodal analysis determine the current in various branches of the n/w.

Sol:- First simplify the n/w

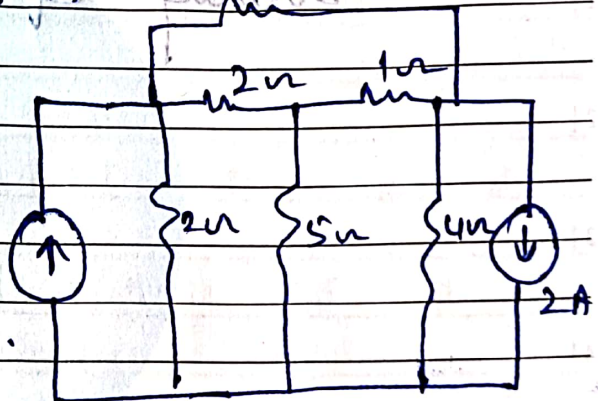
for finding independent nodes & reference nodes (node D).



Now make directions of current across each resistance.

independent nodes - A, B, C

At node A.

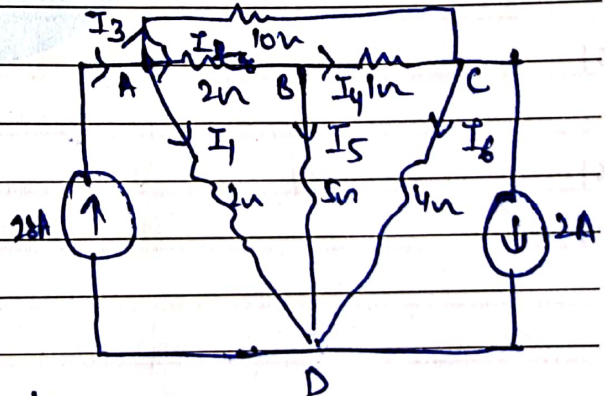

$$V_A \left(\frac{1}{2} + \frac{1}{2} + \frac{1}{10} \right) - \frac{V_B}{2} - \frac{V_C}{10} = 28$$

$$11V_A - 5V_B - V_C = 280 \quad \text{--- (1)}$$


At node B

$$V_B \left(\frac{1}{2} + \frac{1}{5} + 1 \right) - \frac{V_A}{2} - \frac{V_C}{1} = 0$$

Theremin Theorem :-

Theremin theorem states that "any linear circuit containing several voltages & resistances can be replaced by just one single voltage in series with a single resistance connected across the load."

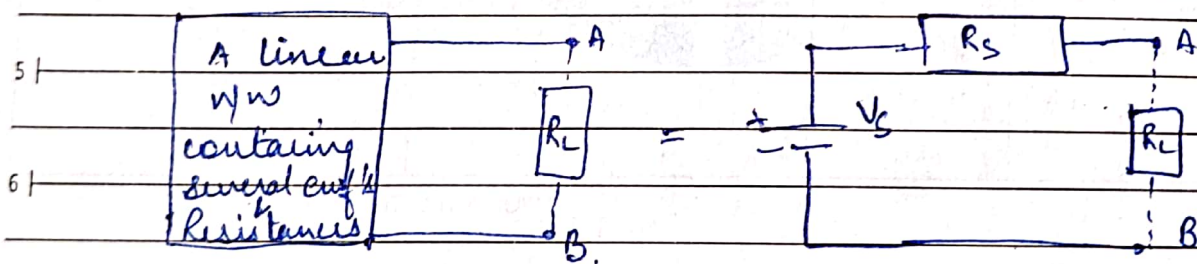It is useful in the circuit analysis of power or battery systems & other inter-connected resistive circuits where it will have an effect on the adjoining part of the circuit.



Steps to solve Theremin Theorem :-

Important Notes


- Step 1:- Identify the load (R_L).
- Step 2:- Remove the load & calculate the open-circuit voltage (V_{TH})

FEBRUARY 2014						
M	T	W	T	F	S	S
				1	2	
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28		

Step 3 :- To calculate Thevenin Impedance (R_{TH}) replace the sources with their internal impedance.

Step 4 :- Construct the Thevenin equivalent circuit by connecting (V_{TH}) in series with (R_{TH}).

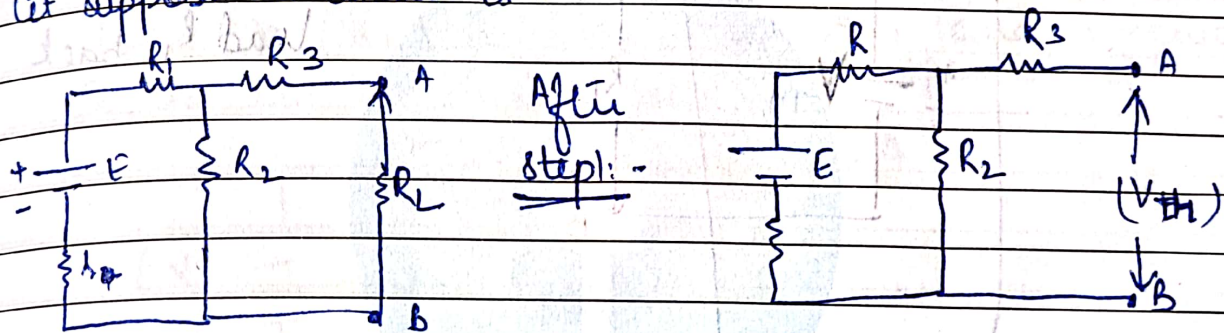After step 1 :- The circuit will be
let suppose the circuit is.



After step 2 :-

To determine open circuit voltage V_{th} b/w terminals A & B. (which is same as voltage across R_L)


First calculate current.

$$I = \frac{E}{R + R_2}$$

Important Notes

The thevenin voltage is -
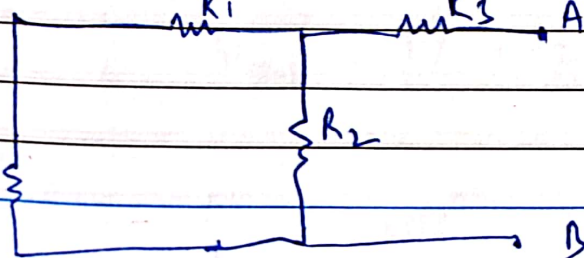
$$V_{TH} = R_2 \times I = R_2 I \text{ (V)}$$



some of voltage is the calculate the circuit is short circuit

if current source is there it is open circuit

JANUARY 2024						
M	T	W	T	F	S	S
6	7	8	2	3	4	5
13	14	15	9	10	11	12
20	21	22	16	17	18	19
27	28	29	23	24	25	26
			30	31		


03

 JANUARY
 FRIDAY

After step 3:-

The circuit will be.
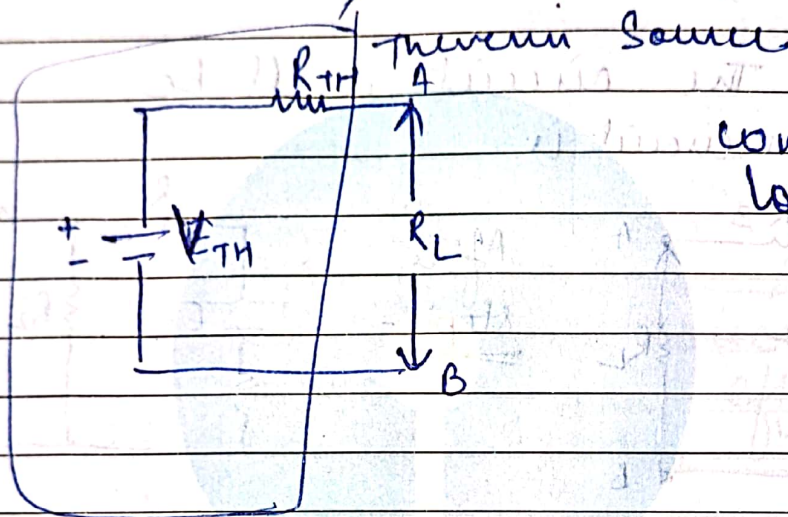
$$R_{TH} = \frac{(r + R_1) R_2}{(r + R_1) + R_2} + R_3$$




Now, determine the current flowing through load resistor R_L by applying Ohm's law.

$$I = \frac{V_{TH}}{R_{TH} + R_L}$$


Important Notes

FEBRUARY 2014						
M	T	W	T	F	S	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28		

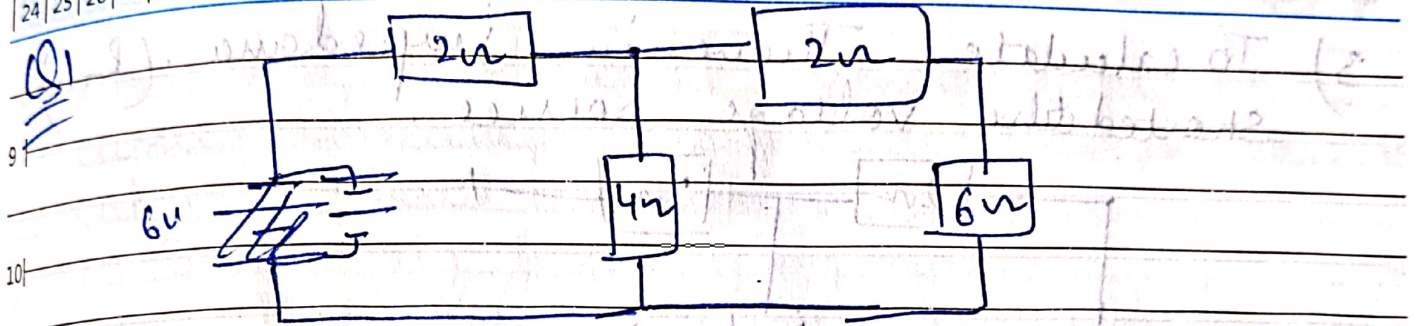

Calculate the current through 6Ω resistor.

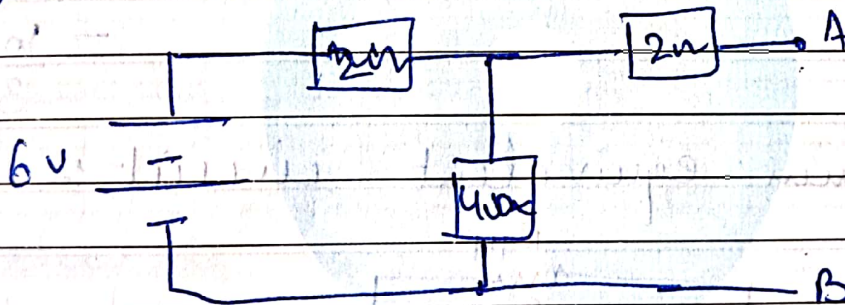Sol:-) First remove the load. Here the load is $(R_L) = 6\Omega$. When the load is removed it is open circuit. So, the circuit will be



2) Now the open circuit voltage is the same as that of the voltage across the resistor of resistance (4Ω) .

So, the current in the circuit is

$$I = \frac{6}{2+4} = 1 \text{ Amp}$$

SUNDAY 05

Important Notes


The Thevenin voltage is

$$V_{TH} = I \times 4 = 4V$$

06

 JANUARY
 MONDAY

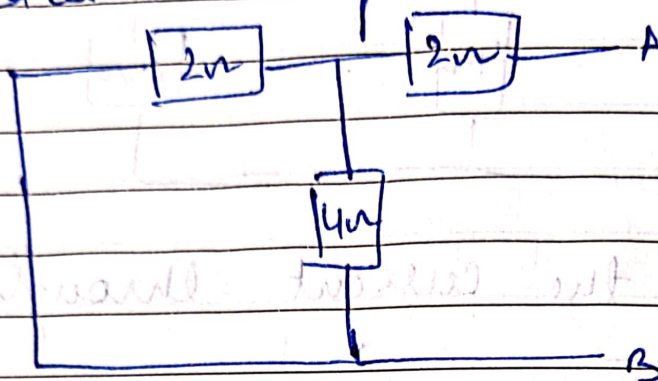
3) To calculate Thevenin impedance (R_{TH})
 shorted the voltage source.



$$R_{TH} = [2+2] \parallel [4] = \left[\frac{2 \times 4}{2+4} + 2 \right] = \left[\frac{4}{3} + 2 \right]$$

$$= \frac{10}{3} \Omega = 3.34 \Omega$$

4) Thevenin equivalent circuit :-

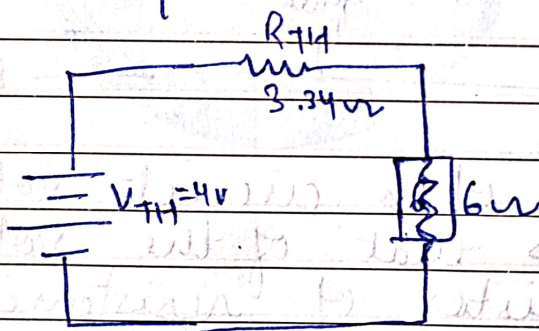

Now, to calculate the current across load 6Ω .

Apply Ohm's law.


$$I = \frac{V_{TH}}{R_{TH} + R_L} = \frac{4}{3.34 + 6} = \frac{4}{9.34}$$

$$= 0.43 \text{ Amp.}$$


FEBRUARY 2014											
M	T	W	T	F	S	S	1	2	3	4	5
3	4	5	6	7	8	9	10	11	12	13	14
17	18	19	20	21	22	23	24	25	26	27	28



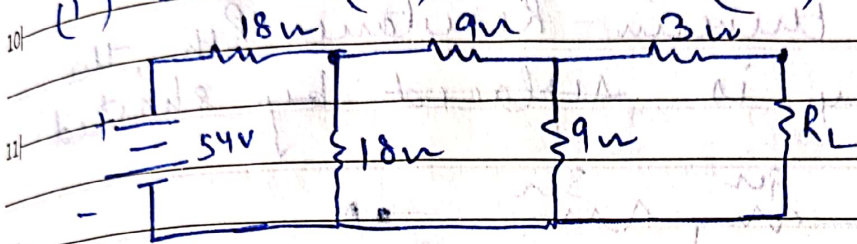Q For a n/w shown determine the current flowing through R_L when the value of load resistance is (i) $3\ \Omega$ (ii) $6\ \Omega$ (iii) $9\ \Omega$



1) Remove load.

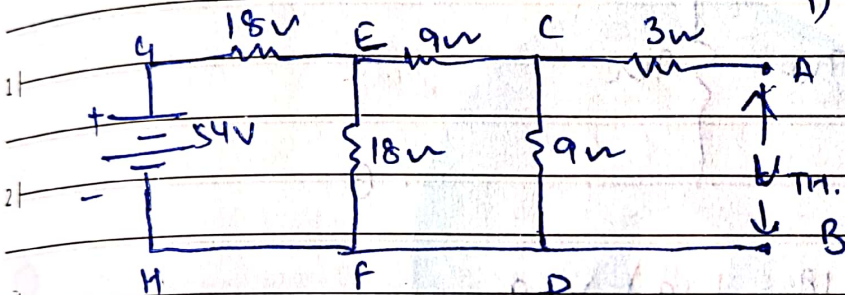

2) Calculate V_{TH} .

$$R = 18 + \frac{(9+9) \times 18}{(9+9) \times 18} = 27\ \Omega$$

Current supplied by battery 54V

$$I = \frac{V_{TH}}{R} = \frac{54}{27} = 2\text{A}$$

Current ~~across~~ flowing through circuit. ECD or CD.

$$= 2 \times \frac{(9+9)}{(9+9) \times 18} = 1\text{A}$$

Important Notes




JANUARY 2014						
M	T	W	T	F	S	S
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

V_{TH} across AB or CD.

$$V_{TH} = 1 \times 9 = 9V$$

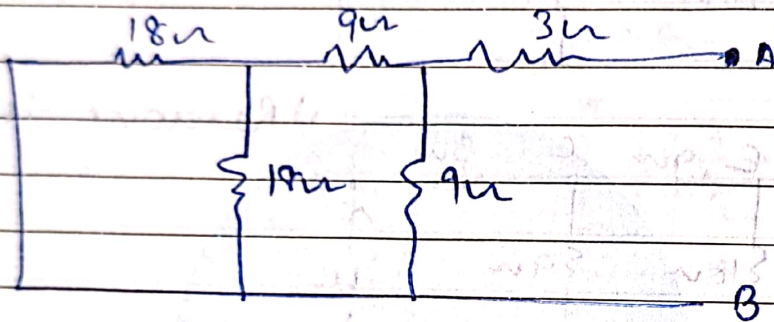b) To determine Thevenin Resistance R_{th} , the source battery is replaced by shorted.



$$R_{th} = \left(\frac{18 \times 18}{18 + 18} + 9 \right) \times 9$$


$$+ 3$$

$$\left(\frac{18 \times 18}{18 + 18} + 9 \right) \times 9 + 3$$

$$= \frac{(9 + 9) \times 9}{(9 + 9) + 9} + 3 = \frac{18 \times 9}{27} + 3 = 9\Omega$$

Now circuit is reduced to

Important Notes

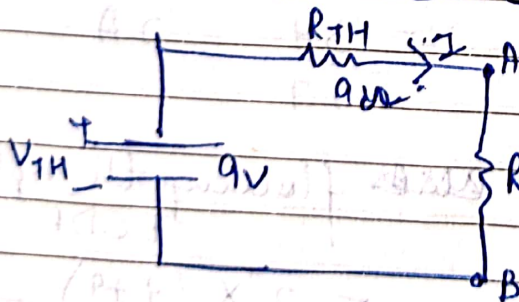

FEBRUARY 2014						
M	T	W	T	F	S	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28		

(i) when $R_L = 3 \Omega$

$$I_1 = \frac{V_{TH}}{R_{TH} + R_L} = \frac{9.3}{9 + 3} = 0.75 \text{ A}$$

(ii) when $R_L = 6 \Omega$


$$I_2 = \frac{9}{9 + 6} = \frac{9}{15} = 0.6 \text{ A}$$

(iii) when $R_L = 9 \Omega$

$$I_3 = \frac{9}{9 + 9} = \frac{9}{18} = 0.5 \text{ A}$$


Q. A bridge network ABCD is arranged as follows. Resistances b/w terminals A-B, B-C, C-D, D-A and B-D are 10, 30, 15, 20 and 40 Ω resp. A 2 volt battery of negligible internal resistance is connected b/w terminals A & C. Determine the value and direction of the current in 40 Ω resistor by applying Thevenin theorem.

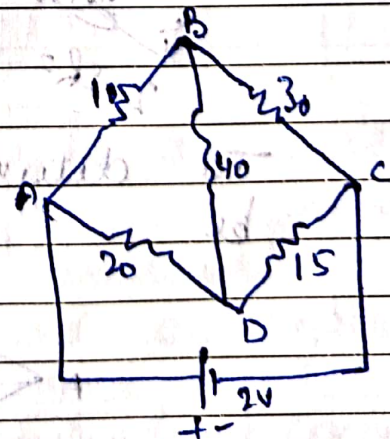Sol: - Step 1: - Remove 40 Ω & calculate E_{TH} or V_{TH} .



Important Notes
So the circuit will be:

JANUARY 2014						
M	T	W	T	F	S	S
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

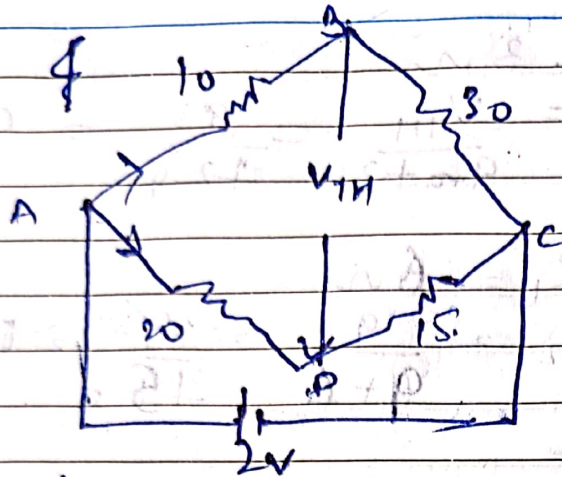

Current in branch ABC $I_1 = \frac{2}{10+30} = 0.05A$

" " " ADC $I_2 = \frac{2}{20+15} = 0.057A$

Voltage at point B, $V_B = 2 - 0.05 \times 10 = 1.5V$


" " " D $V_D = 2 - 0.057 \times 20 = 0.85V$

$V_A - V_B = IR$

$2 - IR =$

V_{TH} across terminal B & D
 $V_{TH} = 1.5 - 0.85 = 0.64$

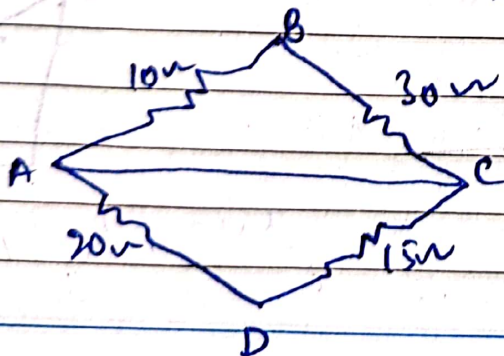To determine R_{TH} , the circuit will be



Important Notes




FEBRUARY 2014						
M	T	W	T	F	S	S
3	4	5	6	7	1	2
10	11	12	13	14	8	9
17	18	19	20	21	15	16
24	25	26	27	28	22	23

$$R_{TH} = \frac{10 \times 30}{10 + 30} + \frac{20 \times 15}{20 + 15}$$

$$= 7.5 + 8.57 = 16.07 \Omega$$

Final circuit will be

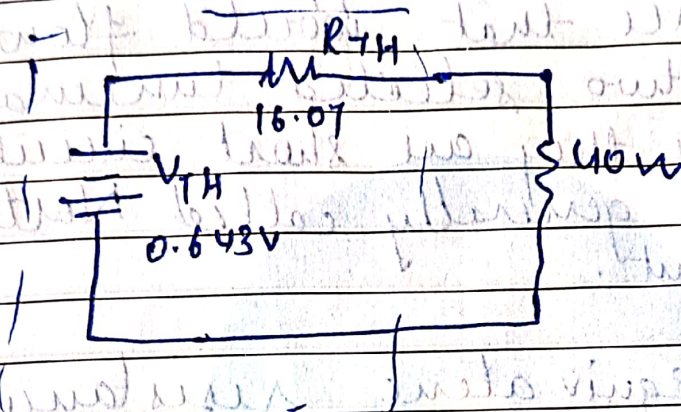

$$I = \frac{0.643}{16.07 + 40} = 11.467 \text{ mA}$$

NORTON'S Theorem :-

This theorem states that at each time

The current flowing through a resistance

Important Notes

connected across any two terminals of a n/w can be determined by replacing the whole n/w by an equivalent circuit of a current source having a current of

JANUARY 2014						
M	T	W	T	F	S	S
6	7	1	2	3	4	5
13	14	8	9	10	11	12
20	21	15	16	17	18	19
27	28	22	23	24	25	26
		29	30	31		

of I_N in H_{lt} parallel with a resistance R_N .

where I_N = The short circuited current supplied by the source that would flow b/w the two selected terminals when they are short circuited. It is generally called Norton's current.

R_N = The equivalent resistance of the n/w as seen from the two terminals with all other emf sources replaced by their internal resistances & current sources replaced by open circuit. It is generally called Norton's resistance.

Steps to determine Norton's equivalent circuit

Important Notes

Step 1 :- Short circuit the terminals across which the load resistor is connected & calculate the current.


FEBRUARY 2014						
M	T	W	T	F	S	S
	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28		



which would flow b/w them. This is the current I_n .

Step 2:- Redraw the n/w each voltage source by a short circuit in series with its internal resistance, if any & each current source by an open ~~source~~ circuit in parallel with its internal resistance.

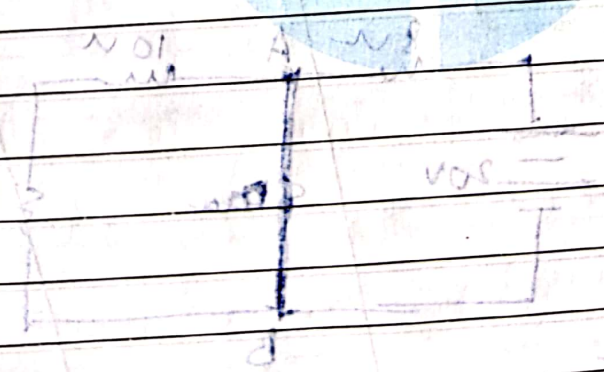Step 3:- Determine the resistance R_n of the n/w as seen from the n/w terminals.




Important Notes




JANUARY 2014						
M	T	W	T	F	S	S
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

17 JANUARY FRIDAY

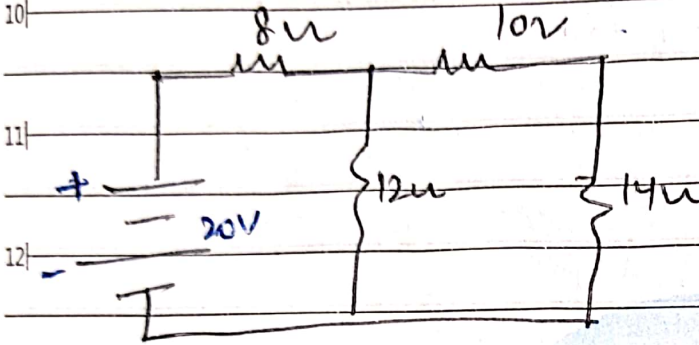
Q Using Norton's Theorem determine the current in 12Ω resistor in the n/w shown.



Step 1 - Identify load & remove it

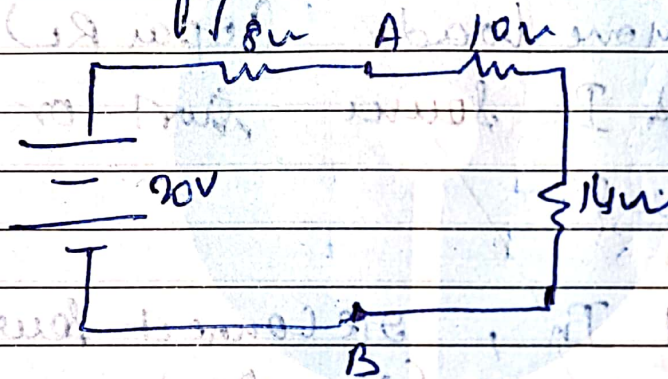

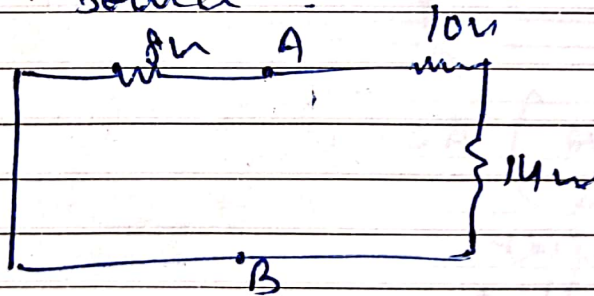Step 2 - Calculate R_N , by short circuiting voltage source



Important Notes


$$R_N = \frac{8 \times (10 + 14)}{8 + (10 + 14)} = 6\Omega$$

FEBRUARY 2014						
M	T	W	T	F	S	S
					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28		




Step 3:- Bring back the voltage source

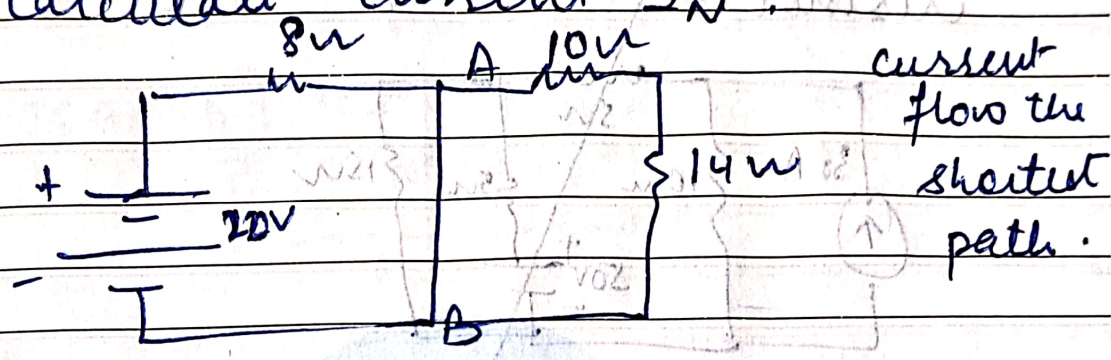& terminals A & B be short circuited to calculate current I_N .



$$I_N = \frac{V}{R} = \frac{20}{8} = 2.5A$$

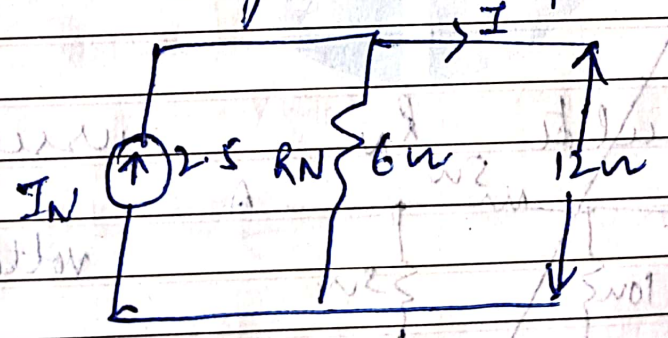Step 4:- Draw the equivalent Norton circuit by drawing I_N & R_N & load R_L be back



$$I = I_N \times \frac{R_N}{R_N + R_L} = 2.5 \times \frac{6}{6+12}$$

Important Notes


$$= 2.5 \times \frac{6}{18} = 0.833A$$




M	T	W	T	F	S	S
6	7	1	2	3	4	5
13	14	8	9	10	11	12
20	21	15	16	17	18	19
27	28	22	23	24	25	26
		29	30	31		

Newton's Numerical

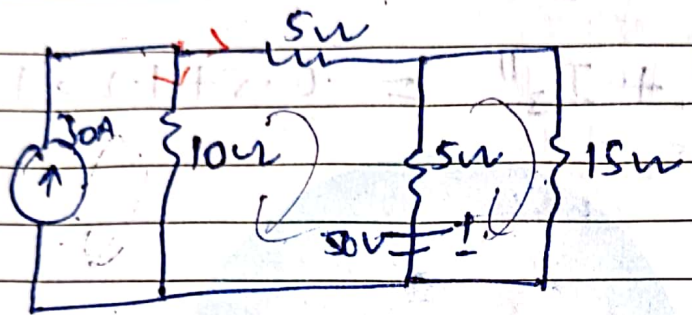
For -w n/w, draw a Newton's equivalent circuit & determine the current flowing through 15Ω resistor.



Step 1:- Identify load

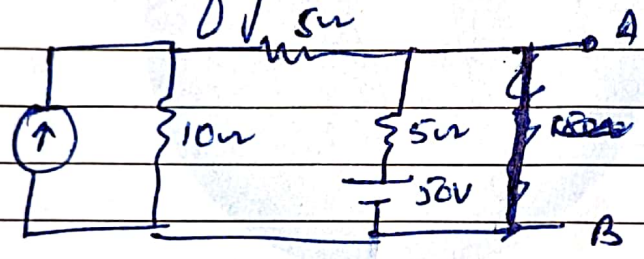

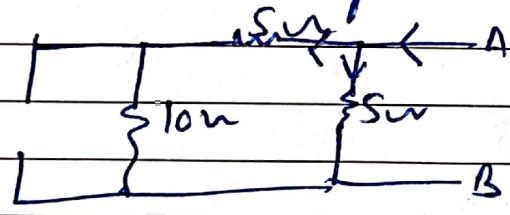Step 2:- Calculate R_N by shorting the voltage source & open the current source




Important Notes
 $\frac{20}{15} = \frac{4}{3}$
 $\frac{20}{15} = \frac{4}{3}$

$$R_N = \frac{(5 + 10) \times 5}{(5 + 10) + 5} = \frac{15 \times 5}{15 + 5} = \frac{75}{20} = 3.75 \Omega$$



	T	W	T	F	S	S
4	5	6	7	8	9	
11	12	13	14	15	16	
18	19	20	21	22	23	
25	26	27	28			

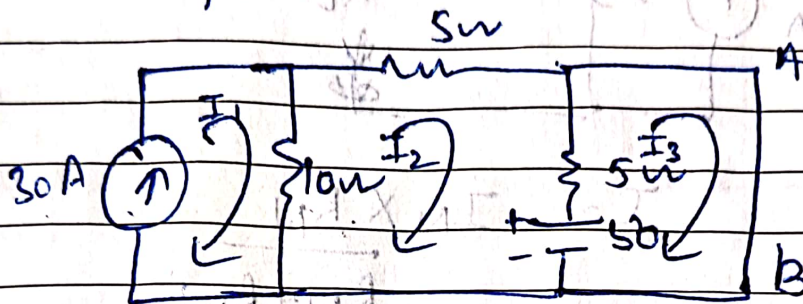Step 1: - Calculate I_N by bring back the original sources & short circuit the A & B pt.



$$30(I_1 - I_2) = 0 \quad I_1 = 30A$$

$$30I_1 - 30I_2 = 0 \quad \text{--- (1)}$$

$$5I_2 + 5(I_2 - I_3) + 50 + 10(I_2 - I_1) = 0$$

$$5I_2 + 5I_2 - 5I_3 + 50 + 10I_2 - 10I_1 = 0$$

$$20I_2 - 10I_1 - 5I_3 = -50 \quad \text{--- (2)}$$

$$-50 + 5(I_3 - I_2) = 0$$

$$5I_3 - 5I_2 = 50 \quad \text{--- (3)}$$

Solving (1)

Important Notes

$$20I_2 - 10 \times 30 - 5I_3 = -50$$

$$20I_2 - 300 - 5I_3 = -50$$

$$20I_2 - 5I_3 = 250 \quad \text{--- (2)}$$

Solving (2) & (3)


$$I_2 = 20A$$

$$I_3 = 30A$$



JANUARY 2014						
M	T	W	T	F	S	S
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

Step 4:-

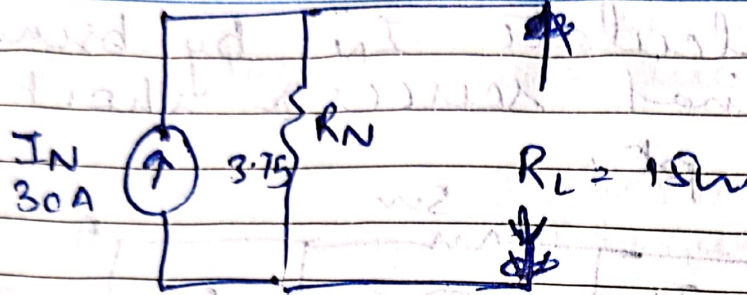

$$I = \frac{I_N \times R_N}{R_N + R_L}$$

$$I = \frac{30 \times 3.75}{3.75 + 15}$$

$$I = \frac{30 \times 3.75}{18.75} = 6A$$

Important Notes


3	4	5	6	7
10	11	12	13	14
17	18	19	20	21
24	25	26	27	28

01

FEBRUARY
SATURDAY

Current division ~~Method~~ Rule CDR

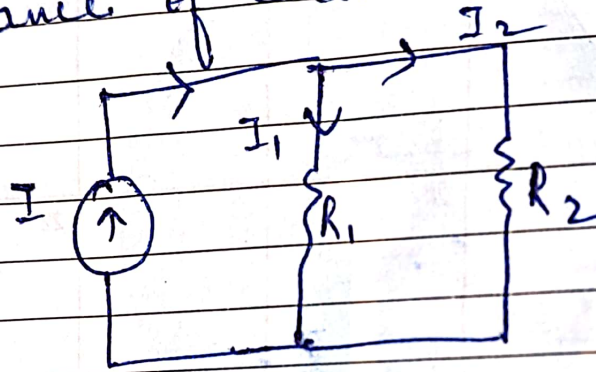The current division rule states that in a parallel circuit, the total current entering the junction divides among the parallel branches in an amount inversely proportional to the resistance or impedance of each branch.



$$I_1 = I \times \frac{R_2}{R_1 + R_2}$$

opposite resist current resistance.

$$I_2 = I \times \frac{R_1}{R_1 + R_2}$$

SUNDAY 02

Important Notes

→ You apply current division rule when you are sure of the total current entering a parallel n/w & wish to easily calculate the current in one branch.

$$\frac{1}{3} + \frac{1}{6} = \frac{1}{3} + \frac{1}{6}$$

MARCH 2014						
T	W	T	F	S	S	
4	5	6	7	1	2	
11	12	13	14	8	9	
18	19	20	21	15	16	
25	26	27	28	22	23	
				29	30	




FEBRUARY
MONDAY

03

Voltage Divider Rule :- (VDR)

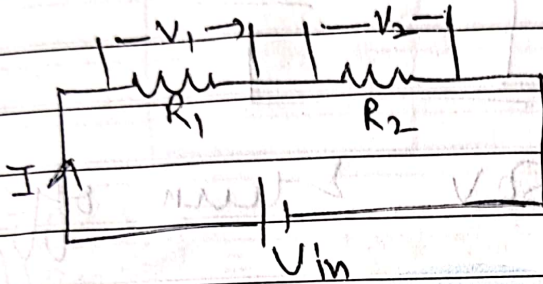Find out voltage across resistor :-
Resistors connected in series.



$I = I_1 + I_2$ (same current)
Voltage is divided
 $V = V_1 + V_2$

$$V_{in} = V_1 + V_2$$

$$V_1 = IR_1 \quad \text{--- (1)}$$

$$V_2 = IR_2 \quad \text{--- (2)}$$

$$V_{in} = I(R_1 + R_2)$$

$$I = \frac{V_{in}}{R_1 + R_2}$$

Putting the value of I.

$$\text{Voltage across } R_1, \quad V_1 = IR_1 = \frac{R_1}{R_1 + R_2} V_{in}$$

$$V_2 = IR_2 = \frac{R_2}{R_1 + R_2} V_{in}$$


Important Notes

FEBRUARY 2014							S	1	2
M	T	W	T	F	S	S	1	2	
3	4	5	6	7	8	9	1	2	
10	11	12	13	14	15	16	3	4	
17	18	19	20	21	22	23	5	6	
24	25	26	27	28			7	8	


Super Position Theorem

1) If there are two or more than two sources of emf acting simultaneously in a linear bilateral n/w, the current flowing through any section is the algebraic sum of all the currents which should flow in that section if each source of emf were considered separately. All other sources are replaced for the time being by their internal resistances.

Consider the circuit

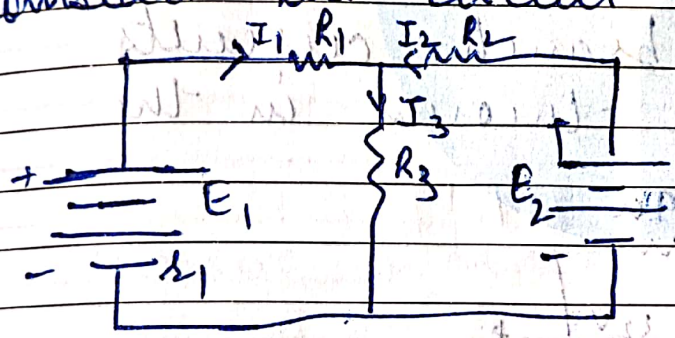

All to super position theorem

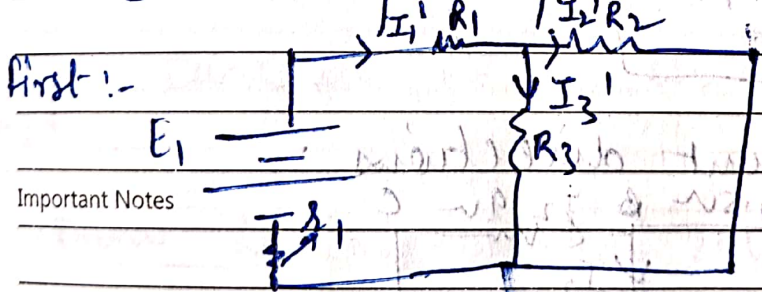


1) First one source is considered i.e. E_1

Important Notes

2) Then source 2 is considered i.e. E_2 .



JANUARY 2024						
M	T	W	T	F	S	S
6	7	1	2	3	4	5
13	14	8	9	10	11	12
20	21	15	16	17	18	19
27	28	22	23	24	25	26
		29	30	31		

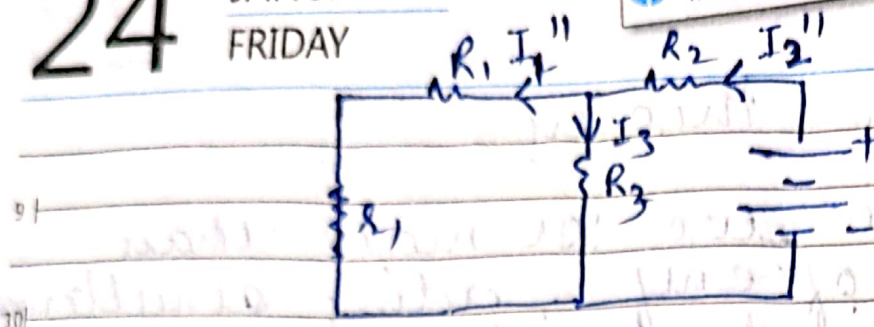


Now Actual flow of current in various sections :-

$$I_1 = I_1' - I_1''$$

$$I_2 = I_2' - I_2''$$


$$I_3 = I_3' + I_3''$$

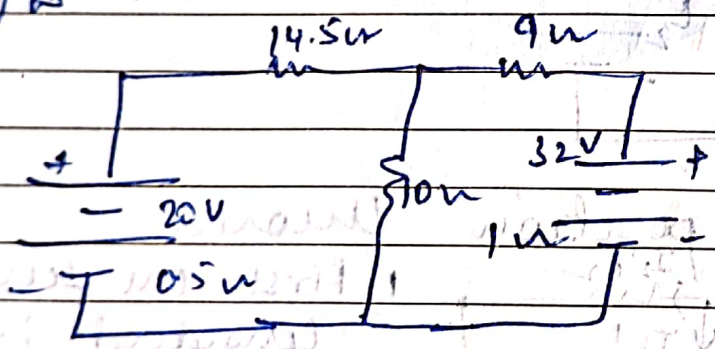Q Determine the branch currents by superposition theorem in the circuit.



First draw current directions.


Important Notes

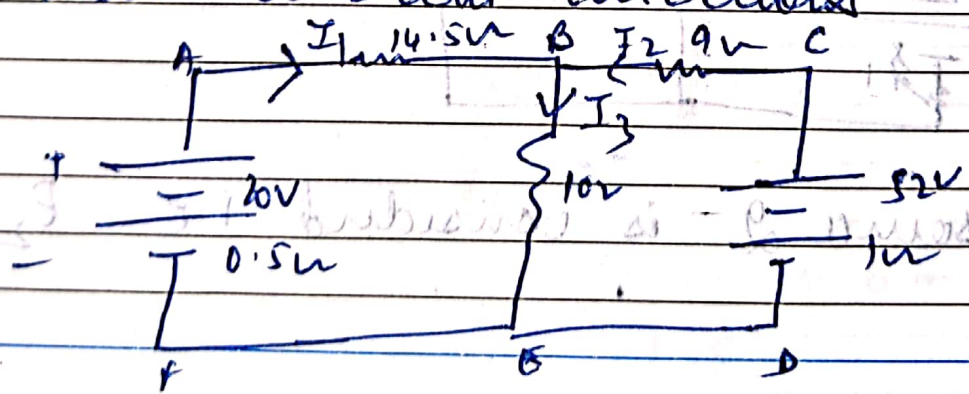



M	T	W	T	F	S	S
					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28		

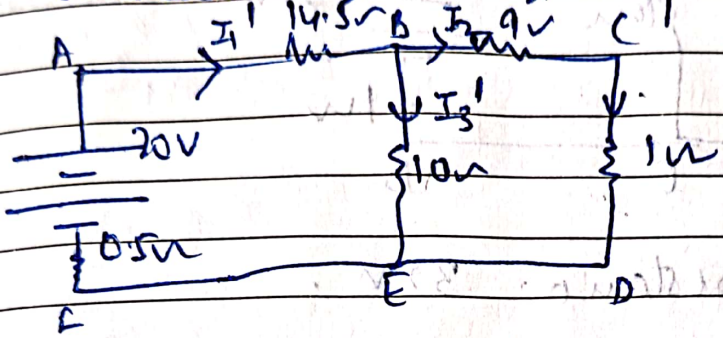Acc. to super position theorem
First consider 20V & replace 32V



Total resistance across 20V

$$R_{total} = 14.5 + 0.5 + \frac{10 \times (9+1)}{10+(9+1)} = 20\Omega$$

Current supplied by the source = $I_1' = \frac{V}{R_{total}}$

$$I_1' = \frac{20}{20} = 1A$$

Current in branch BCDE = $I_2' = 1 \times \frac{10}{10+10}$

$$= 0.5A$$

Current in branch BE = $I_3' = 1 \times \frac{10}{10+10} = 0.5A$


SUNDAY 26

Now replace battery 20V & put 32V.



JANUARY 2014						
M	T	W	T	F	S	S
6	7	8	9	10	11	12
13	14	15	16	17	18	19
20	21	22	23	24	25	26
27	28	29	30	31		

27 JANUARY MONDAY

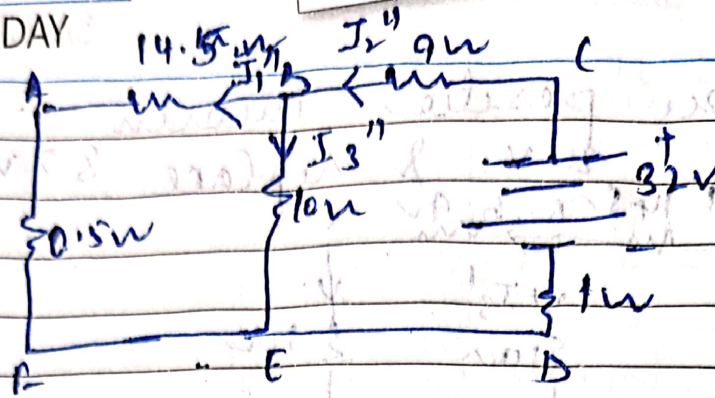

Total resistance = 32Ω

$$R_{total} = 9 + 1 + \frac{15 \times 10}{15 + 10} = 16 \Omega$$

Current supplied by source

$$I_2'' = \frac{32}{16} = 2A$$

Current in branch BAFE

$$I_1'' = 2 \times \frac{10}{10 + 15} = 0.8A$$

Current in branch BE

$$I_3'' = 2 \times \frac{15}{10 + 15} = 1.2A$$

Important Notes

FEBRUARY 2014						
T	W	T	F	S	S	
4	5	6	7	8	9	
11	12	13	14	15	16	
18	19	20	21	22	23	
25	26	27	28			




Acc to Super position, the actual currents will be

$$I_1 = I_1' - I_1'' = 1 - 0.8 = 0.2 \text{ A } A-B$$

$$I_2 = I_2' - I_2'' = 0.5 - 2.0 = -1.5 \text{ A } B-B$$
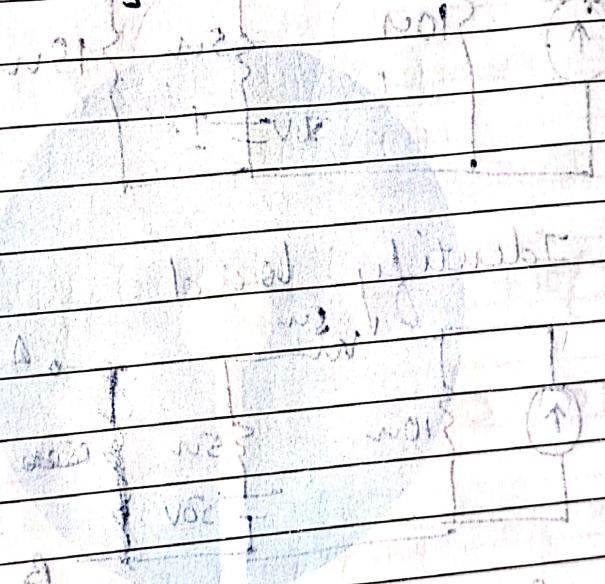
$$I_3 = I_3' + I_3'' = 0.5 + 1.2 = 1.7 \text{ A } B-E$$




Important Notes

$2 \times (0.1 + 2) = 0.4$
 $2 \times (0.1 + 2) = 0.4$
 $2 \times (0.1 + 2) = 0.4$




M	T	W	T	F	S	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

Super position Problems

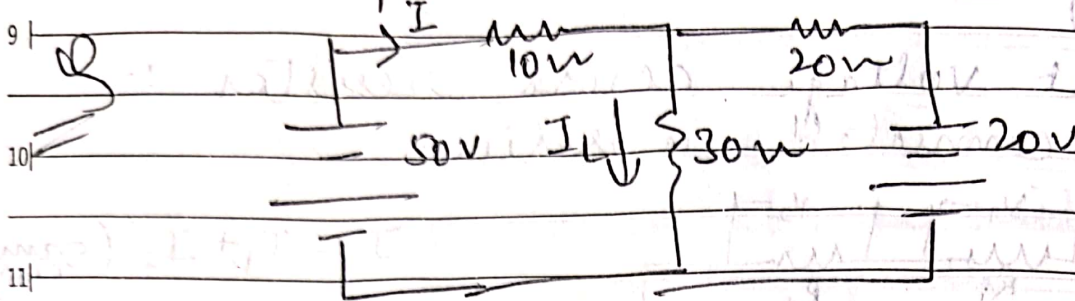


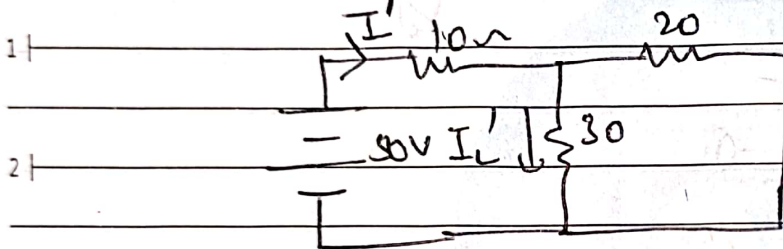Step 1:- Consider 50V & turn off all other source



$$30\Omega \parallel 20\Omega = \frac{30 \times 20}{30 + 20} = \frac{600}{50} = 12\Omega$$

Redraw circuit

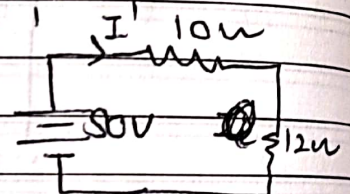

$$I' = \frac{V}{R} = \frac{50}{10 + 12} = 2.27A$$

By using current division rule

$$I'_L = I' \times \frac{20}{20 + 30}$$


Important Notes

$$= 2.27 \times \frac{20}{20 + 30}$$


$$I'_L = 0.908$$

MARCH 2014						
M	T	W	T	F	S	S
31				1	2	
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

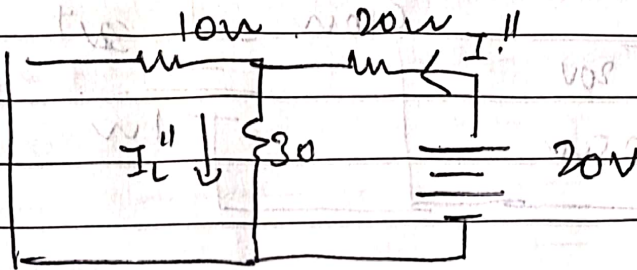Consider 20V voltage source & turn off all other sources.


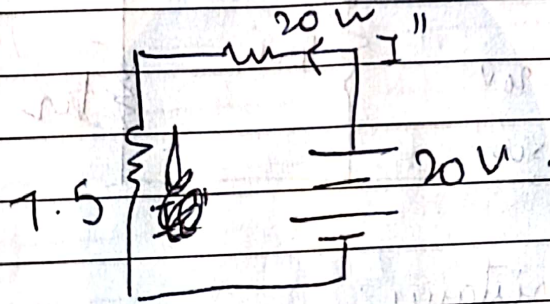
$$10 \parallel 30 = \frac{10 \times 30}{10 + 30} = 7.5 \Omega$$



$$I'' = \frac{20}{20 + 7.5} = 0.72 \text{ A}$$

To find I_L'' apply C.D.R

$$I_L'' = I'' \times \frac{10}{10 + 30}$$

$$= 0.72 \times \frac{10}{10 + 30}$$

(opposite resistor which is in parallel)


$$I_L'' = 0.18 \text{ A}$$

Important Notes

$$I_L = I_L' + I_L''$$


$$I_L = 0.908 + 0.18 = 1.088 \text{ A}$$

MARCH 2014						
M	T	W	T	F	S	S
31					1	2
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

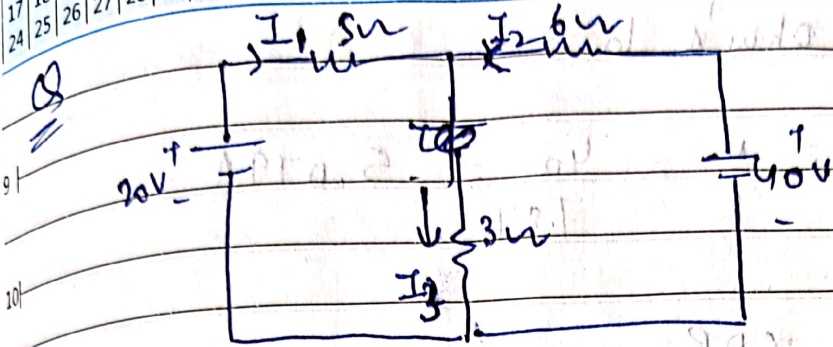

Find the current through 3Ω resistor using super position theorem.

Consider 1st source -

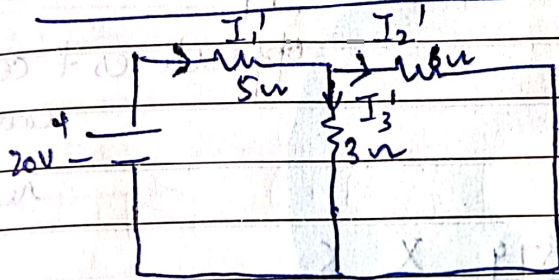

$$\text{Total resistance} = \frac{6 \times 3}{6+3} + 5$$

$$= \frac{18}{9} + 5 = 2 + 5 = 7\Omega$$

Apply Ohm's law


$$I_1 = \frac{V}{R} = \frac{20}{7} = 2.8 \text{ A}$$

Apply CDR

$$I_3' = 2.8 \times \frac{6}{3+6}$$

$$= 2.8 \times \frac{6^2}{93} = 1.866 \text{ A}$$

Now consider source 2.

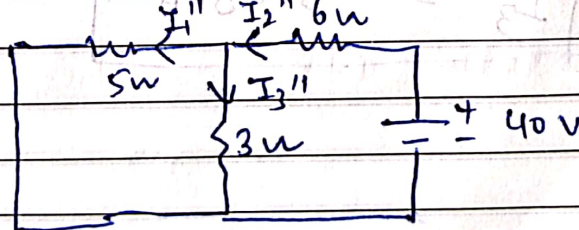

$$\text{Total resistance} = \frac{5 \times 3}{5+3} + 6 = \frac{15}{8} + 6 = 7.875 \Omega$$



FEBRUARY 2014						
M	T	W	T	F	S	S
3	4	5	6	7	8	9
10	11	12	13	14	15	16
17	18	19	20	21	22	23
24	25	26	27	28	29	30

Apply Ohm's law.

9 |

$$I_2'' = \frac{V}{R} = \frac{40}{7.87} = 5.079 \text{ A}$$

10 |

11 |

Apply CDR.

12 |

~~$I_3'' = I_2''$~~

1 |

$$I_3'' = I_{\text{total}} \times \frac{\text{opposite resistance}}{\text{opposite res} + \text{current carrying res.}}$$

2 |

3 |

$$I_3'' = 5.079 \times \frac{5}{5+3}$$

4 |

5 |

$$= 5.079 \times \frac{5}{8} = 3.17 \text{ A}$$

6 |

$$I_3 = I_3' + I_3''$$

$$= 1.866 + 3.17$$

$$I_3 = 5.036 \text{ A}$$

Important Notes