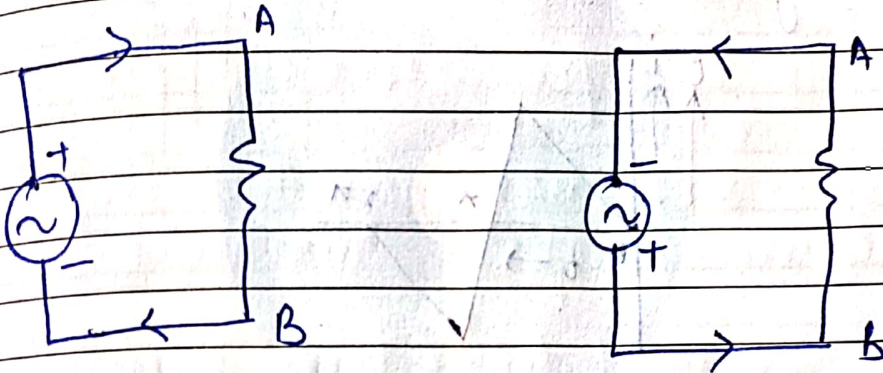


## Chapter 2

### AC circuits


#### Alternating voltage & current :-

A voltage that changes its polarity & magnitude at regular intervals of time is called alternating voltage.



wave shape of the source voltage

or waveform.

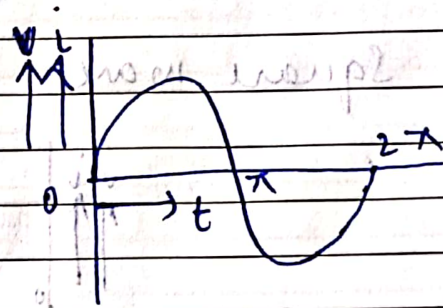


Important Notes

The alternating voltage or current vary in different manner accordingly their wave shapes are named in different ways such as :-


M	T	W	T
5	6	7	8
12	13	14	15
19	20	21	22
26	27	28	29

22 MAY THURSDAY


1) Irregular wave

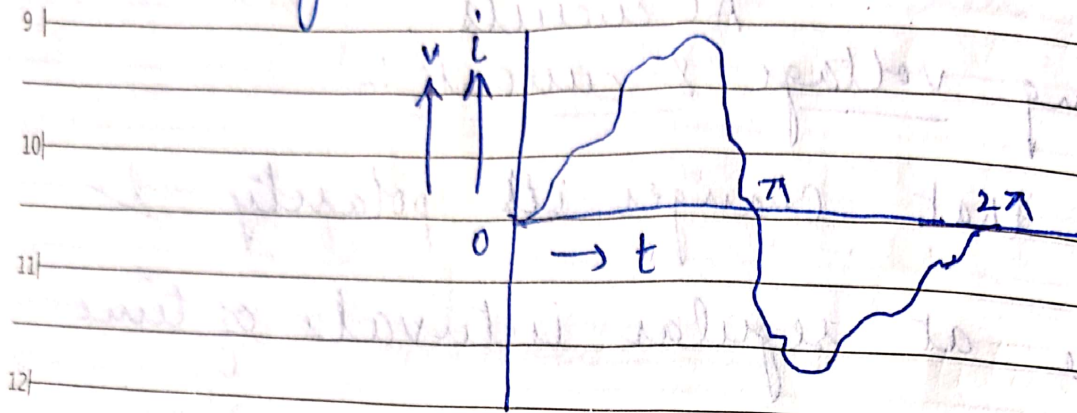

2) Triangular wave

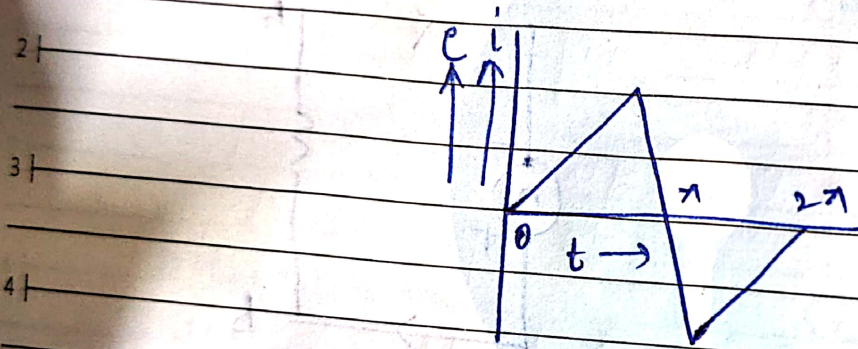

3) Square wave

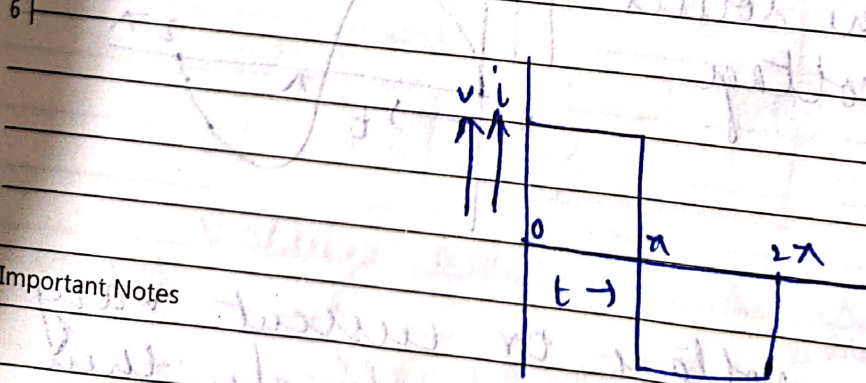

Important Notes

4) Periodic wave



MAY 2014						
M	T	W	T	F	S	S
5	6	7	1	2	3	
12	13	14	8	9	10	
19	20	21	15	16	17	
26	27	28	22	23	24	
			29	30	31	

24 MAY  
SATURDAY

## Sinusoidal Alternating Quantity :-

An alternating quantity (i.e. voltage or current) which varies according to sine of angle  $\theta$  ( $\theta = \omega t$ ) is known as sinusoidal alternating quantity.

- (1) Sinusoidal voltages & currents produce low iron & copper losses in a.c. rotating machines & transformers. This improves the efficiency of ac machines.
- (2) The sinusoidal voltages & current offer less interference to nearby communication system.
- (3) They produce least disturbance in the electrical circuits.

## Important notes

Important Notes

SUNDAY

- (1) Waveform :- The shape of curve obtained by plotting the instantaneous values of alternating quantity along y-axis

JUNE 2024						
S	M	T	W	T	F	S
						1
						2
						3
						4
						5
						6
						7
						8
						9
						10
						11
						12
						13
						14
						15
						16
						17
						18
						19
						20
						21
						22
						23
						24
						25
						26
						27
						28
						29

and time (or angle ( $\theta = \omega t$ ) along x-axis is called waveform

(2) Instantaneous value :- The value of an alternating quantity i.e voltage or current at any instant is called its instantaneous value & is represented by  $v$  or  $i$ . resp.

(3) Cycle :- when an alternating quantity goes through a complete set of +ve & -ve values or goes through 360 electrical degrees it is said to have one complete cycle.

(4) Alternation :- One half cycle is called alternation. An alternation spans 180 electrical degree.

(5) Time period :- The time taken in seconds to complete one cycle by an alternating quantity is called time period. It is generally denoted by  $T$ .

(6) Frequency :- The number of cycles made per second by an alternating quantity is called frequency. It is measured in

MAY 2014						
S	M	T	W	T	F	S
5	6	7	1	2	3	4
12	13	14	8	9	10	11
19	20	21	15	16	17	18
26	27	28	22	23	24	25
			29	30	31	

27 MAY TUESDAY

cycles per second or hertz (Hz) & is denoted by  $f$ .

(7) Amplitude:- The maximum value (+ve or -ve) attained by an alternating quantity in one cycle is called its amplitude or peak value or max value. The max value of voltage or current is generally denoted by  $E_m$  or  $V_m$  &  $I_m$  resp.

(1) Relation b/w Time & frequency

Time taken to complete  $f$  cycle = 1 sec

" " " " " " 1 cycle =  $\frac{1}{f}$  sec

$$T = \frac{1}{f} \text{ sec} \quad \text{or} \quad f = \frac{1}{T} \text{ c/s.}$$

tant Notes) Relation b/w frequency & angular velocity

Angular distance covered in one cycle =  $2\pi$  radians





MAY 2014						
M	T	W	T	F	S	S
5	6	7	1	2	3	4
12	13	14	8	9	10	11
19	20	21	15	16	17	18
26	27	28	22	23	24	25
			29	30	31	

29

MAY THURSDAY

Method

Generalised formula of I<sub>av</sub> is  $I_{av} = \frac{\text{Area of alternation}}{\text{base}} = \frac{i_1 + i_2}{2}$

$t = I_{max} \sin \omega t$

$I_{av} = \frac{\text{Area of first half cycle}}{\pi}$

Analytical Method

$$= \frac{1}{\pi} \int_0^{\pi} i \, d\omega t$$

$$= \frac{1}{\pi} \int_0^{\pi} I_{max} \sin(\omega t) \, d(\omega t)$$

$$= \frac{I_{max}}{\pi} \left[ -\cos \omega t \right]_0^{\pi}$$

$$= \frac{I_{max}}{\pi} (-\cos \pi + \cos 0)$$

$$= \frac{-I_{max}}{\pi} [-1 - 1]$$

$$= \frac{2 I_{max}}{\pi}$$

Important Notes

$I_{av} = 0.637 I_m$  (the half cycle)





M		T		W		T		F		S	
MAY 2014											
5	6	7	8	9	10	11	12	13	14	15	16
19	20	21	22	23	24	25	26	27	28	29	30

$$= \frac{I_{max}^2}{2\pi} \int_0^{\pi} (1 - \cos 2\omega t) d\omega t$$

$$= \frac{I_{max}^2}{2\pi} \left[ \omega t - \frac{\sin 2\omega t}{2} \right]_0^{\pi}$$

$$= \frac{I_{max}^2}{2\pi} (\pi - 0)$$

$$= \frac{I_{max}^2}{2\pi} \times \pi$$

$$= \frac{I_{max}^2}{2}$$

$$I_{rms} = \sqrt{\frac{I_{max}^2}{2}}$$

$$I_{rms}^2 = \frac{I_{max}^2}{2}$$


$$I_{rms} = \sqrt{\frac{1}{2}} I_{max}$$

$$I_{rms} = \frac{1}{\sqrt{2}} I_{max}$$

$$(1/\sqrt{2}) \approx 0.707 I_{max}$$


Important Notes

## Phase Angle or Phase Difference

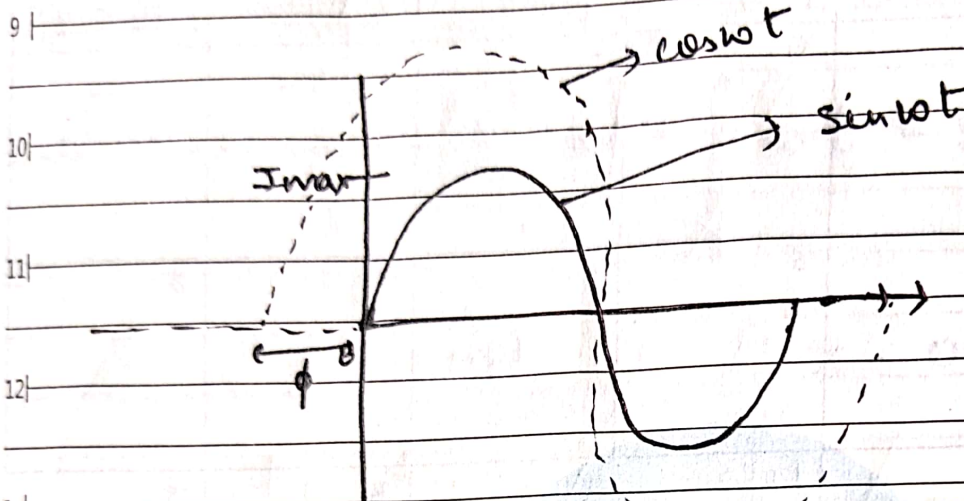
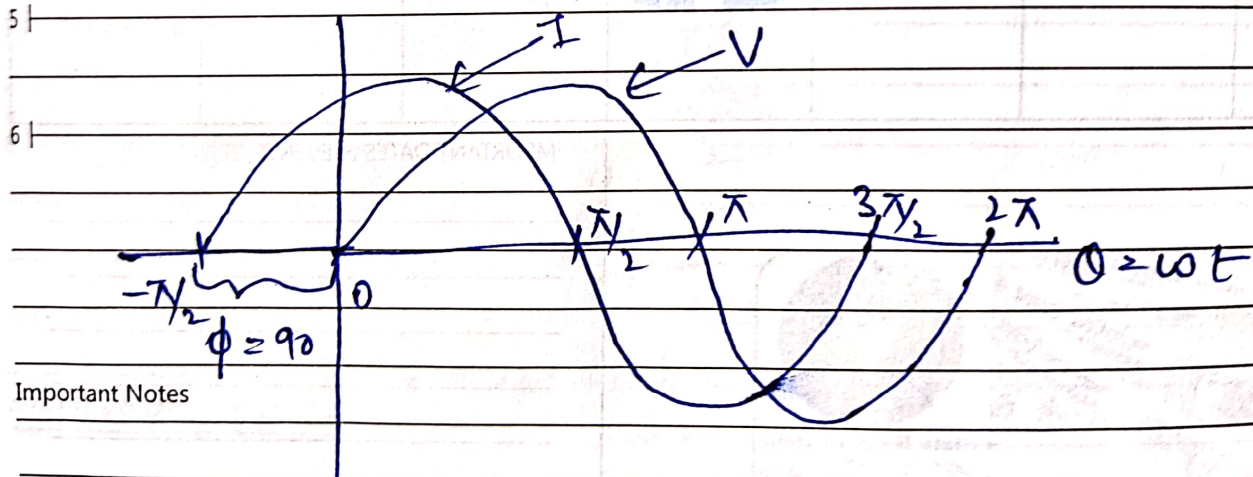
### Phase or Phase Difference

It is the angular shift or time delay between two waves of the same frequency indicating how much one wave leads or lags the other. It is measured in degrees or radians.



Important Notes

JULY 2014						
M	T	W	T	F	S	S
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			

## Altiminals

### Form factor:

The ratio of rms value to average value of an alternating quantity is called form factor.

$$\text{Form factor} = \frac{I_{\text{rms}}}{I_{\text{av}}}$$

for the current varying sinusoidally

$$\text{Form factor} = \frac{I_{\text{rms}}}{I_{\text{av}}} = \frac{I_m / \sqrt{2}}{2 I_m / \pi} = \frac{\pi I_m}{2 \sqrt{2} I_m} = 1.11$$

Peak factor: The ratio of maximum value to rms value of an alternating quantity is called peak factor.

$$\text{Peak factor} = \frac{I_m}{I_{\text{rms}}}$$

for current varying sinusoidally

$$\text{Peak factor} = \frac{I_m}{I_{\text{rms}}} = \frac{I_m}{I_m / \sqrt{2}} = \sqrt{2} = 1.414$$

07 JUNE  
SATURDAY

M	T	W	T	F	S	S
30						
2	3	4	5	6		
9	10	11	12	13		
16	17	18	19	20		
23	24	25	26	27		

Q An alternating current is given by the expression  $i = 50 \sin 628t$ .

Determine (i) max value of current

(ii) rms value of current

(iii) frequency of current

(iv) value of current after  $t = 0.00625$  s

(v) time taken by the current to reach a value of 20 A.

(i)  $I_m = 50$  A

(ii)  $I_{rms} = I_m / \sqrt{2} = 50 / \sqrt{2} = 35.355$  A

(iii)  $\omega = 2\pi f = 628$  or  $f = \frac{628}{2\pi} = 100$  Hz

(iv)  $i = 50 \sin 628 \times 0.00625 = -35.3$  A

(v)  $20 = 50 \sin 628t$

Important Notes

SUNDAY 08

$$\sin 628t = \frac{20}{50} = 0.8$$

$$628t = \sin^{-1} 0.8 = 0.9273$$

$$t = \frac{0.9273}{628} = 1.476 \times 10^{-3} \text{ s}$$

1	2	3	4	5	6
7	8	9	10	11	12
13	14	15	16	17	18
19	20	21	22	23	24
25	26	27	28	29	30
31					


Q An alternating current of 50 Hz has a max value of 200 A. Reckoning time from the instant current is zero & is becoming +ve, calculate

- (i) the instantaneous value after  $1/400$  s.
- (ii) the time taken for the current to reach 150 A for the first & second time.

If the reckoning time is taken from the instant current is max +ve & becoming zero, after what time it will reach to 150 A.

Sol: -  $i = I_m \sin 2\pi ft$

$i = 200 \sin 100\pi t$

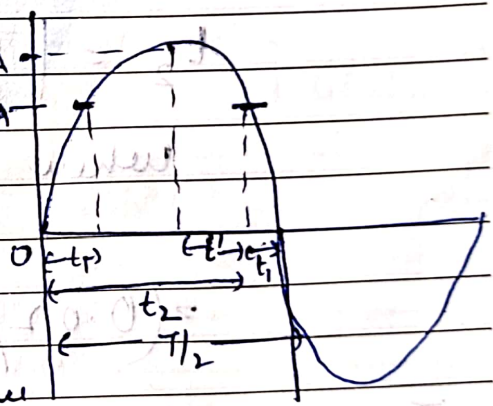

Taking reckoning time from the instant current is zero & becoming positive, the eqn

(i)  $i = 200 \sin 100\pi t$   
 $= 200 \sin \frac{100\pi}{400} = 200 \sin \frac{\pi}{4} = 200 \sin 45^\circ$   
 $= 141.42 \text{ A}$

Important Notes

JUNE 2014						
M	T	W	T	F	S	S
30						
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

(ii) let the current reaches to 150A

for the first time after  $t_1$  sec.

$$200 \sin 100 \pi t_1 = 150$$

$$\sin 100 \pi t_1 = 0.75$$

$$100 \pi t_1 = \sin^{-1} 0.75$$

$$t_1 = 0.84806 / 100 \pi = 2.7 \text{ ms}$$

let the current reaches to 150A  
for the second time after  $t_2$  sec.

$$t_2 = (T/2 - t_1)$$

$$\text{where } T = \frac{1}{f} = \frac{1}{50} = 0.02 \text{ s}$$

$$= (0.02/2) - 2.7 \times 10^{-3} = 7.3 \text{ ms}$$

If the reckoning time is taken from the instant current is max +ve, the current

$$i = I_m \sin (\omega t + 90^\circ) = I_m \cos \omega t$$

$$= 200 \cos 100 \pi t$$

JULY 2014						
	S	S				
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			


Let the current reaches 150A after  $t'$  sec.

$$150 = 200 \cos \pi t' \text{ or } \cos 100\pi t' = 0.75$$

$$100\pi t' = \cos^{-1} 0.75$$

$$100\pi t' = 0.7227 \text{ radians}$$
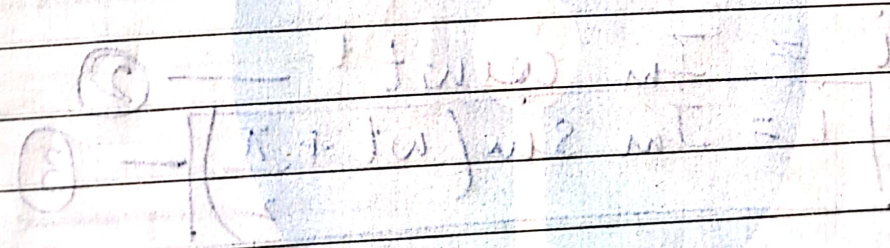
$$t' = \frac{0.7227}{100\pi} = 2.3 \text{ ms}$$





$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

Capacitive reactance  
The capacitor known as  
This is the resistance offered by

M	T	W	T	F	S	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			


Phasor Representation of sinusoidal quantity

$i = I_m \sin \omega t$

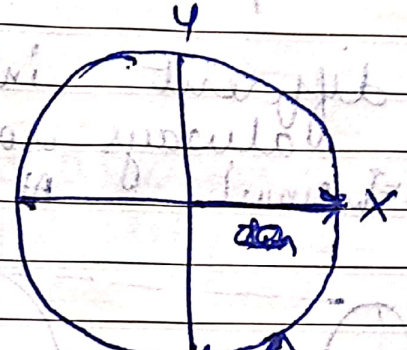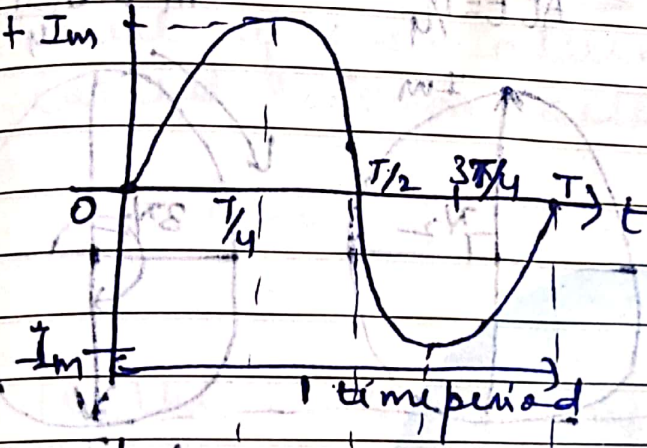

first we consider time

phasor represent of 1/4 quadrant

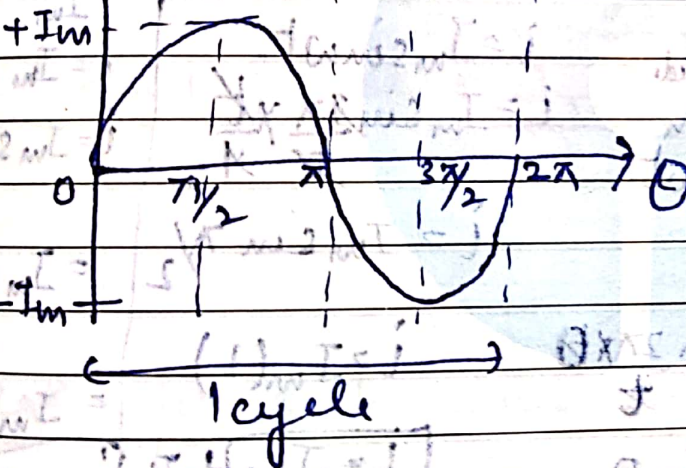

now considering angle 0

phasor representation means the circular representation



Why we use phasor representations - to understand the direction of current.



JUNE 2014						
M	T	W	T	F	S	S
30						
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

05 JUNE THURSDAY

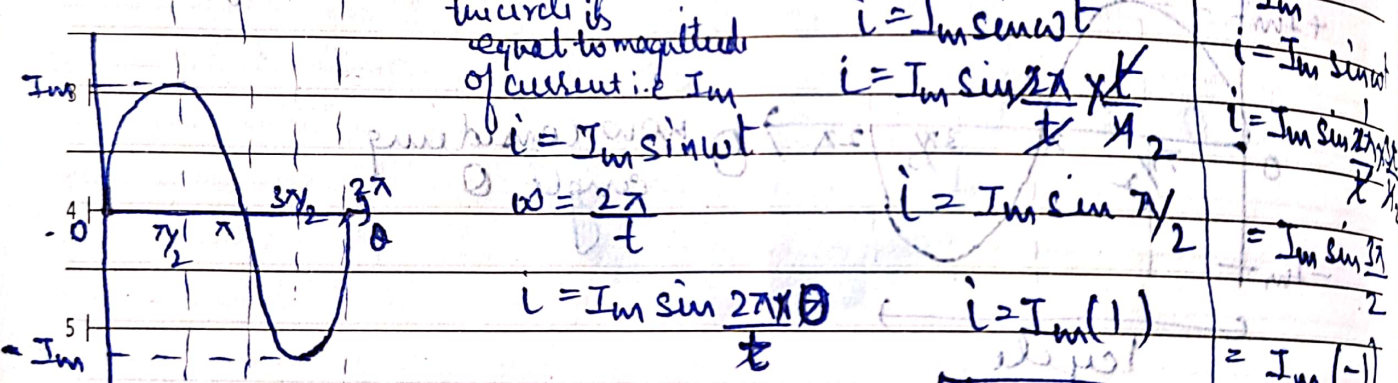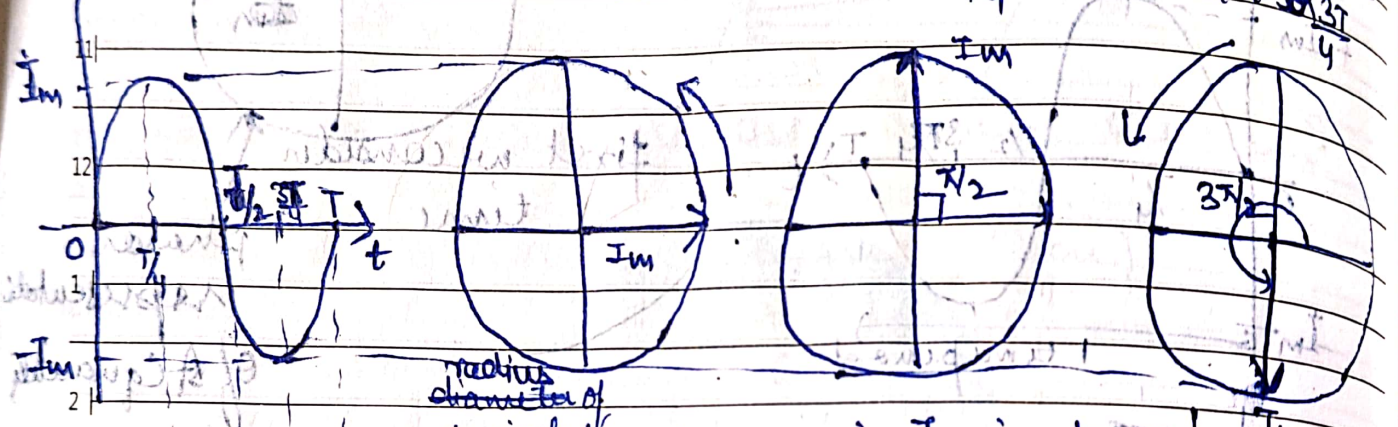To find the direction of current in different intervals of time & vectors  $I_m$  always rotate in anti-clockwise direction.



radius diameter of circle is equal to magnitude of current i.e.  $I_m$

$i = I_m \sin \frac{2\pi \times 0}{T}$

$i = I_m \sin \frac{2\pi \times T/4}{T}$

$i = I_m \sin \frac{2\pi \times T/2}{T}$

$i = I_m \sin \frac{2\pi \times 3T/4}{T}$

$= I_m \sin 3\pi/2$

$i = I_m(1)$


$= I_m(-1)$

$i = I_m \sin 0$

$i = I_m$  at  $t=T/4$        $i = -I_m$  at  $t=3T/4$


let at any time = t

Important Notes

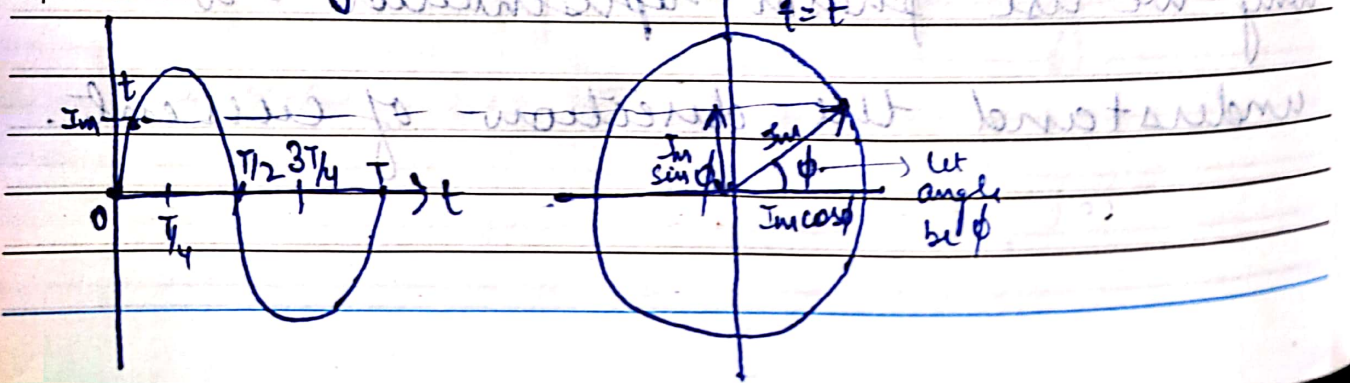
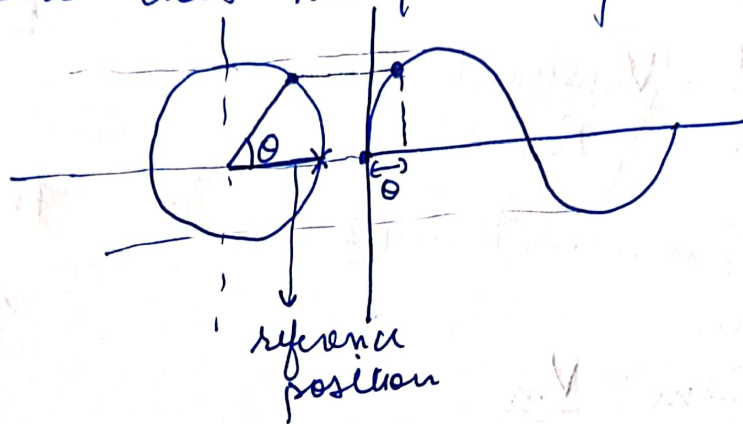
## Concept of Phasor

It gives information about any AC quantity that how much it is from reference position we can represent this AC quantity in vector form




3 cases can be considered, if two quantities are considered :- (one is current & other is voltage) (consider the max & min & draw circle)

Case I voltage is leading by  $\theta$  degree

$$V = V_m \sin \omega t$$

$$i = I_m \sin (\omega t - \theta)$$

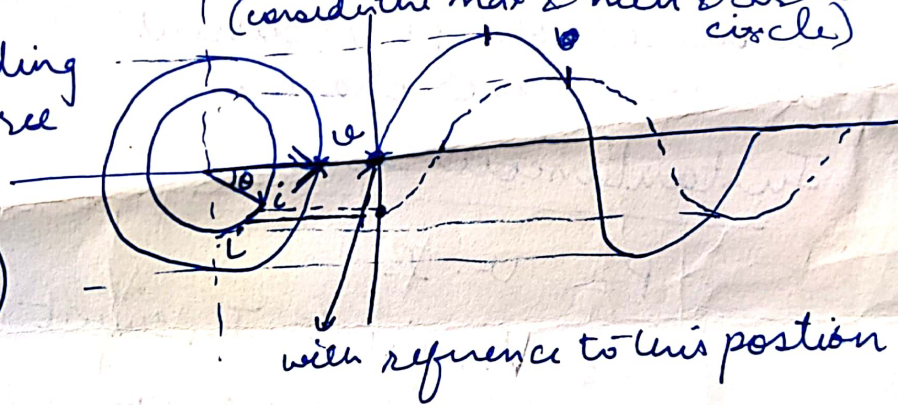


Case II :-

current is leading by  $\theta$  degree


$$V = V_m \sin \omega t$$

$$i = I_m \sin (\omega t + \theta)$$

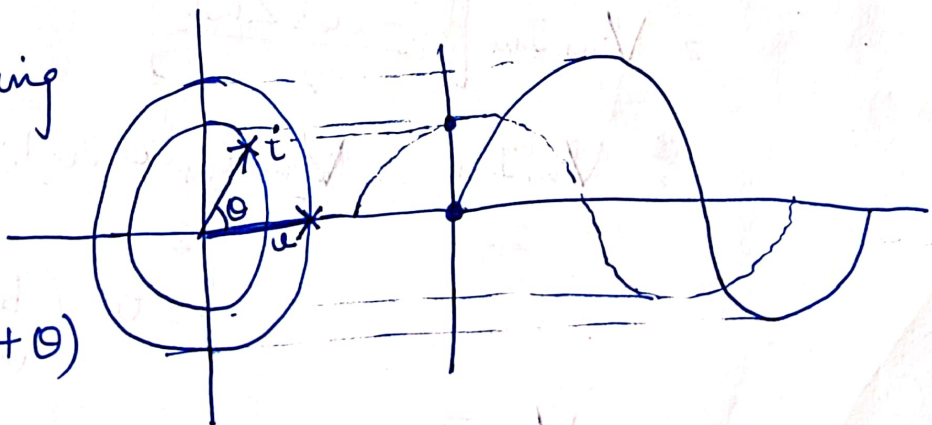

Case III :-

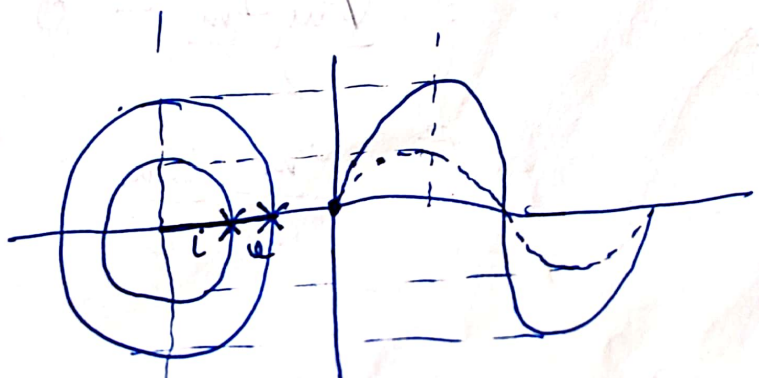Both  $V$  &  $i$  are in same direction.



# AC through Pure Resistive Circuit

In given circuit

$$v = V_m \sin \omega t \quad \text{--- (1)}$$

$$\begin{aligned} i &= \frac{v}{R} = \frac{V_m \sin \omega t}{R} \\ &= I_m \sin \omega t \quad \text{--- (2)} \end{aligned}$$

where

$$I_m = \frac{V_m}{R}$$

Here phase difference is 0 because voltage & current are in same phase.

Instantaneous power

$$P = v \cdot I$$

$$= V_m \sin \omega t \cdot I_m \sin \omega t$$

$$= V_m I_m \sin^2 \omega t$$


$$= V_m I_m \left[ \frac{1 - \cos 2\omega t}{2} \right]$$

$$= \frac{V_m I_m}{2} - \frac{V_m I_m \cos 2\omega t}{2}$$


$\rightarrow 0$  (because Average value of complete cycle is zero)

$$= \frac{V_m I_m}{2} - 0$$

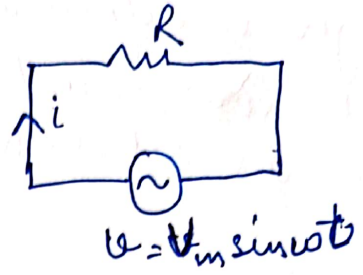
$$= \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = V_{rms} \cdot I_{rms}$$



Phasor

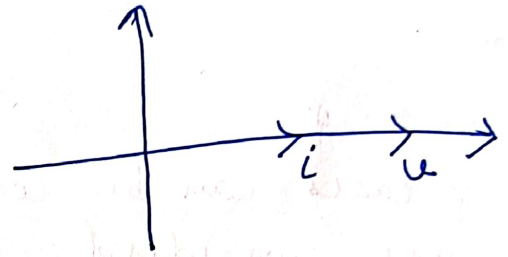

## Phasor :-

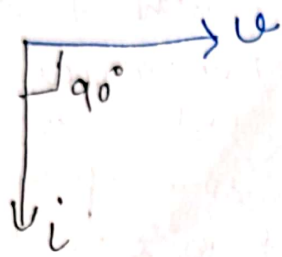

Current is lagging behind the voltage by  $90^\circ$ .

## Power :-

$$P = V \cdot I$$

$$= -V_m \sin \omega t \cdot I_m \cos \omega t$$

Multiply & divide by 2

$$= \frac{V_m I_m}{2} \cdot 2 \sin \omega t \cos \omega t$$

$$(2 \sin A \cos A = \sin 2A)$$

$$P = \frac{V_m I_m}{2} \cdot \sin 2\omega t$$

$\rightarrow 0$


## Average Power :-

$$P_{avg} = \frac{V_m I_m}{2} \cdot 0$$

$$P_{avg} = 0$$


because again Average Power of complete cycle is 0.

## Waveform :-

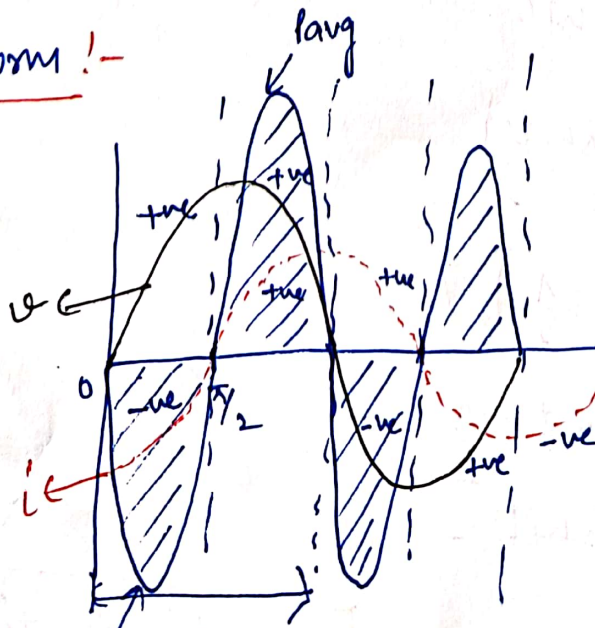

$$P_{avg} = 0 \text{ (for cycle)}$$

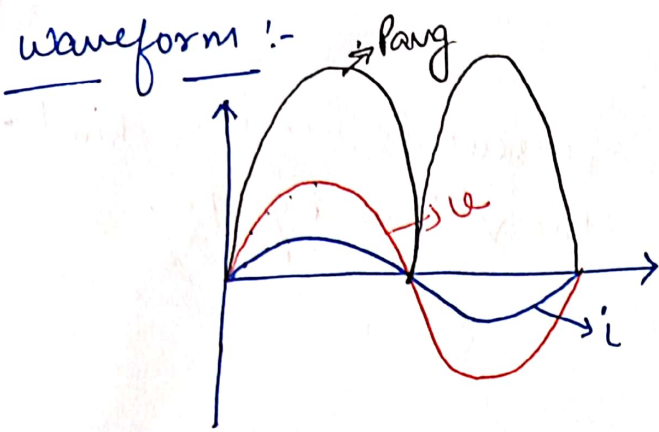In the first half voltage is +ve & current is -ve, so the first half cycle is further divided into two half cycles for power calculation.



In the first half cycle +ve values of voltage multiply with +ve values of current so waveform is +ve for lang & in second half cycle -ve value of voltage multiply with -ve value of current, so -ve & -ve becomes +ve, so lang is +ve in the next half cycle as well.

### AC through Pure Inductive Circuit:-

Given:-

$$v = V_m \sin \omega t \quad \text{--- (1)}$$

Emf in inductor

$$e = -L \frac{di}{dt}$$

$$v = -e = L \frac{di}{dt}$$

$$\frac{di}{dt} = \frac{v}{L} = \frac{V_m \sin \omega t}{L}$$

Integrating both sides

$$i = \frac{V_m}{L} \int \sin \omega t \cdot dt$$

$$i = \frac{V_m}{L} \left( \frac{-\cos \omega t}{\omega} \right)$$

$$i = \frac{V_m \sin \left( \omega t - \frac{\pi}{2} \right)}{\omega L}$$

$$i = I_m \sin \left( \omega t - \frac{\pi}{2} \right) \quad \text{--- (2)}$$

$$i = -I_m \cos \omega t \quad \text{--- (3)}$$

where

$$I_m = \frac{V_m}{\omega L}$$

$$\frac{V_m}{I_m} = \omega L = X_L$$

Inductive reactance is the resistance offered by the inductor. It is known as inductive reactance.

JUNE 2014						
M	T	W	T	F	S	S
30						
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

## AC through Pure Capacitive Circuit

$$v = V_m \sin \omega t \quad \text{--- (1)}$$

Charge

$$q = CV$$

$$= C V_m \sin \omega t$$

and

$$i = \frac{dq}{dt} = \frac{d}{dt} [C V_m \sin \omega t]$$

$$i = C V_m \omega \cos \omega t$$

$$i = I_m \cos \omega t \quad \text{--- (2)}$$

$$i = I_m \sin \left( \omega t + \frac{\pi}{2} \right) \quad \text{--- (3)}$$

where

$$I_m = C V_m \omega$$

$$\frac{V_m}{I_m} = \frac{1}{\omega C} = X_C$$


This is the resistance offered by the capacitor known as Capacitive Reactance.

Important Notes

### Instantaneous Power


$$P = v \cdot i = V_m \sin \omega t \cdot I_m \cos \omega t$$

$$P = \frac{V_m I_m}{2} \sin 2\omega t$$

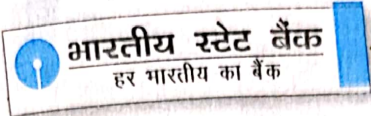

JULY 2014						
S	S					
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			

### Phasor

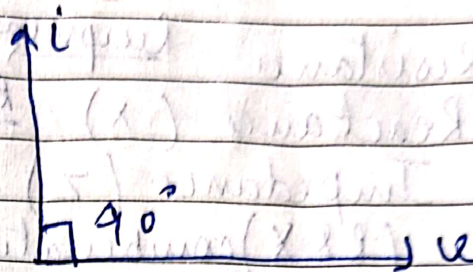


(current is leading by 90° from voltage)

### Average Power

$$P_{avg} = \frac{V_m I_m}{2} \sin 2\omega t$$

$$= \frac{V_m I_m}{2} \cdot 0$$

$$P_{avg} = 0$$

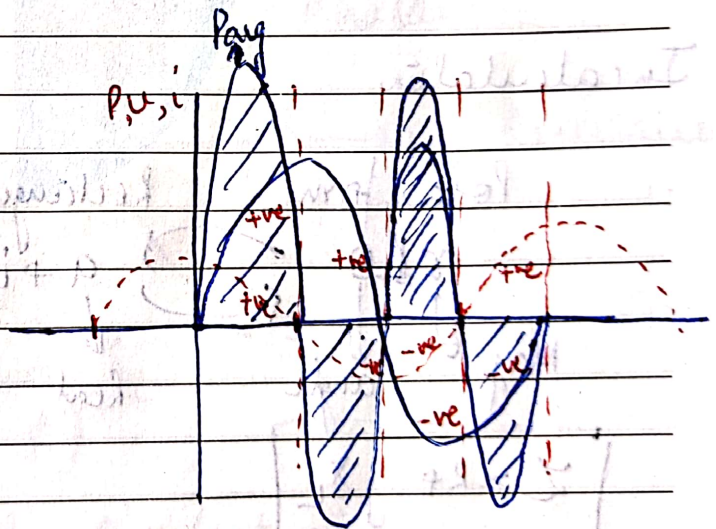

Important Notes

M	T	W	T	F	S	S
30						
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29						

Numericals:-

- Q An a.c circuit consists of pure resistance of  $10\ \Omega$  & is connected across an ac supply of  $230\text{V}$ ,  $50\text{Hz}$ .
- Calculate
- (1) Current
  - (2) Power consumed
  - (3) Write down the eq. for voltage & current.

(1)  $I = \frac{V}{R} = \frac{230}{10} = 23\text{A}$

(2)  $P = VI = 230 \times 23 = 5290\text{W}$

(3)  $V_m = \sqrt{2} V$ ;  $I_m = \sqrt{2} I$

$= \sqrt{2} \times 230$ ,  $I_m = \sqrt{2} \times 23$

$V_m = 325.2\text{V}$ ,  $I_m = 32.53\text{A}$

$\omega = 2\pi f = 2\pi \times 50 = 314.16\text{ rad/s}$

Important Notes

$v = V_m \sin \omega t$

$= 325.27 \sin 314.16 t$

$i = I_m \sin \omega t$

$= 32.53 \sin 314.16 t$



JULY 2014						
S	S	F	T	W	Th	F
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29	30	31				

An inductive coil having negligible resistance & 0.1 henry inductance is connected across 200V, 50Hz supply. Find.

(1) Inductive reactance

(2) Rms value of current

(3) Power

(4) eq<sup>n</sup> for voltage & current

Sol: -

(1)  $X_L = \omega L$

$2\pi f L = 2\pi \times 50 \times 0.1$

$= 31.416 \Omega$

(2)  $I = \frac{V}{X_L} = \frac{200}{31.416} = 6.366 \text{ A}$

(3)  $P = VI$

(4)  $V_m = \sqrt{2} V$ ,  $I_m = \sqrt{2} I$

Important Notes

$V_m = \sqrt{2} \times 200$ ,  $I_m = \sqrt{2} \times 6.366$

$= 282.84 \text{ V}$

$I_m = 282.8 \text{ A}$



JUNE 2014						
S	M	T	W	T	F	S
30						
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29						

$$\omega = 2\pi f = 2\pi \times 50 = 314 \text{ rad/s}$$

$$v = V_m \sin \omega t$$

$$= 282.84 \sin 314 t$$

$$i = I_m \sin \left( \omega t - \frac{\pi}{2} \right)$$

$$= 9 \sin (314 t - \pi/2)$$

Q3. A capacitor has a capacitance of 30 micro farad. Find its capacitive reactance for freq<sup>s</sup> of 25 & 50 Hz. Find i in each case

the current if the supply voltage is 440V.

Sol:- Capacitance =  $30 \times 10^{-6}$  F.  
Supply voltage = 440 V

When supply frequency  $f_1 = 25$  Hz

$$X_{C_1} = \frac{1}{\omega C_1} = \frac{1}{2\pi \times 25 \times 30 \times 10^{-6}}$$

$$= 212.2 \Omega$$

JULY 2014						
M	T	W	T	F	S	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			

भारतीय स्टेट बैंक  
हर भारतीय का बैंक

178-187 DAYS Wk 26

14

JUNE  
FRIDAY

27

$$I_1 = \frac{V}{X_{C1}} = \frac{440}{212.2} = 2.073 \text{ A}$$

When supply freq  $f_2 = 50 \text{ Hz}$

$$X_{C2} = \frac{1}{\omega_2 C} = \frac{1}{2\pi \times 50 \times 30 \times 10^{-6}}$$

$$= 106.1 \Omega$$

$$I_2 = \frac{V}{X_{C2}} = \frac{440}{106.1} = 4.146 \text{ A}$$

M	T	W	T	F	S	S
30						
1	2	3	4	5	6	7
8	9	10	11	12	13	14
15	16	17	18	19	20	21
22	23	24	25	26	27	28
29						

### Concept of Impedance

- 9 | Resistance Reciprocal Conductance
- 10 | Reactance (X) Reciprocal Susceptance
- 11 | Impedance (Z) Reciprocal Admittance
- (R & X) combination is known as Impedance

### 12 | Impedance

$$Z = R + jX_L \Rightarrow \sqrt{R^2 + X_L^2} = |Z| \quad \text{Magnitude}$$





$$\text{Angle } \angle Z = \tan^{-1} \left( \frac{X_L}{R} \right)$$

$$Z = R - jX_C$$

### Calculation

Polar form

Rectangular form

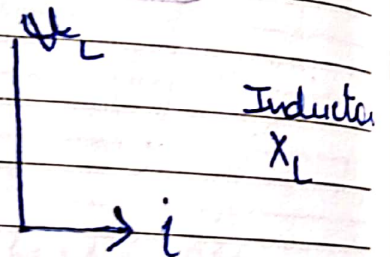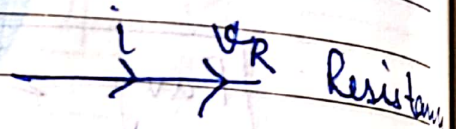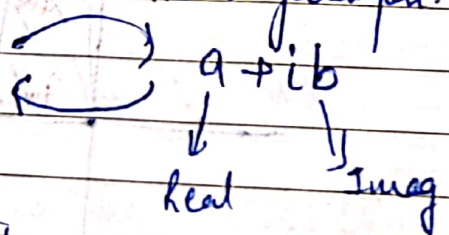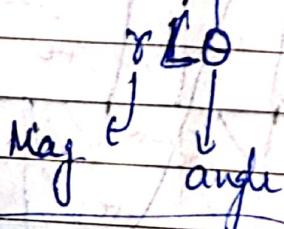


Important Notes

$$Z = R + jX_L$$

$$Z = R - jX_C$$

Combine both

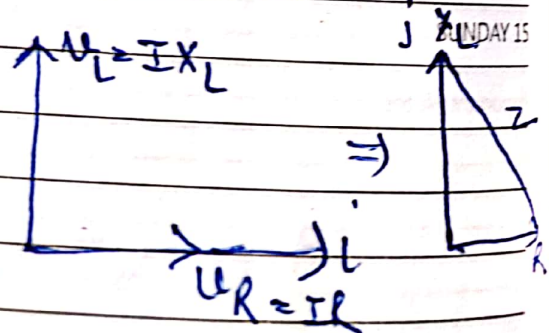

					S	S
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			


AC through Series R-L circuit

$$V = V_m \sin \omega t \quad \text{--- (1)}$$

$$\vec{V} = \vec{V}_R + \vec{V}_L$$

$$\vec{I}Z = \vec{I}R + \vec{I}X_L$$

$$\vec{Z} = \vec{R} + \vec{X}_L$$

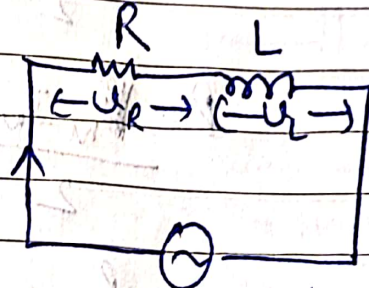

$$V = V_m \sin \omega t$$

Magnitude  $|Z| = \sqrt{R^2 + X_L^2}$

Angle  $\phi = \tan^{-1} \left( \frac{X_L}{R} \right)$  } Impedance.

$$V = V_m \sin \omega t \quad \text{--- (1)}$$

$$i = I_m \sin (\omega t - \phi) \quad \text{--- (2)}$$


Phase:

Power:

$$P = V \cdot I$$

$$P = V_m \sin \omega t \cdot I_m \sin (\omega t - \phi)$$

Inductor  $i_L$

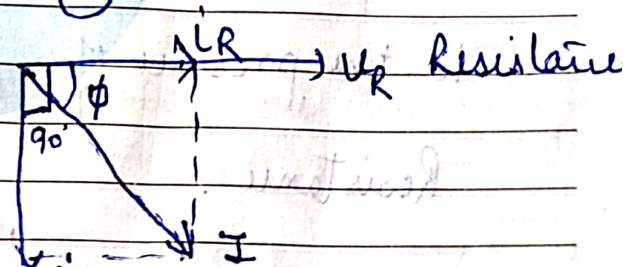

$$= \frac{V_m I_m}{2} 2 \sin \omega t \cdot \sin (\omega t - \phi)$$

Important Notes

$$= \frac{V_m I_m}{2} \left[ \cos (\omega t - \omega t + \phi) \right. \\ \left. - \cos (\omega t + \omega t - \phi) \right]$$

$$\left[ 2 \sin A \sin B = \cos (A - B) - \cos (A + B) \right]$$

30	31	JUNE 2014		
2	3	4	5	6
9	10	11	12	13
16	17	18	19	20
23	24	25	26	27

17

JUNE TUESDAY

$$P = \frac{V_m I_m}{2} [\cos \phi - \cos (2\omega t - \phi)]$$


$$P = \frac{V_m I_m}{2} \cos \phi - \frac{V_m I_m}{2} \cos (2\omega t - \phi)$$

$$P_{avg} = \frac{V_m I_m}{2} \cos \phi$$

$$P_{avg} = V_{rms} I_{rms} \cos \phi$$

$$= V \cdot I \cos \phi$$

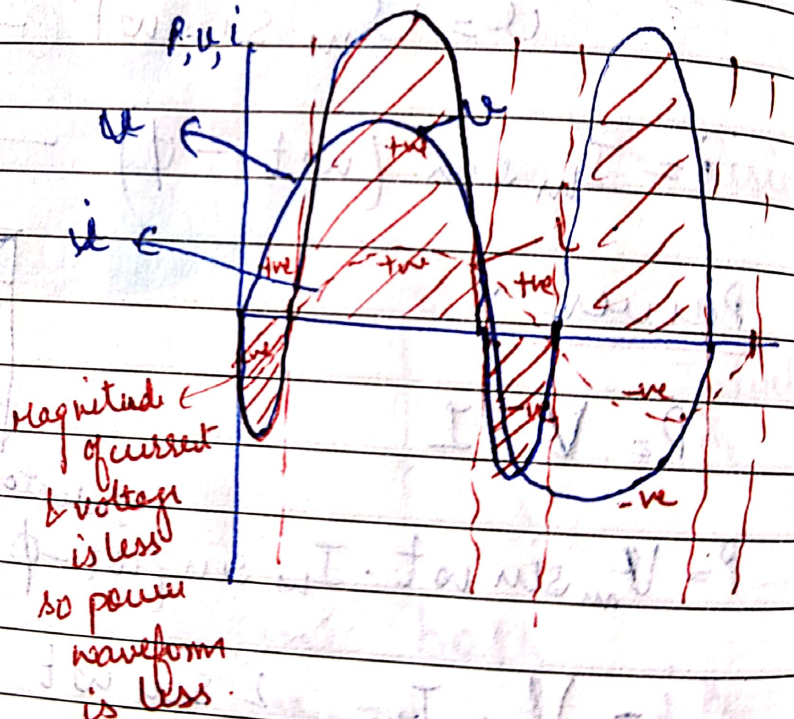This power is due to the presence of Resistance.



ant Notes

## AC through series R-C circuit

$$\vec{V} = \vec{V}_R + \vec{V}_C$$

$$\vec{I}Z = \vec{I}R + \vec{I}X_C$$

$$|Z| = \sqrt{R^2 + X_C^2}$$

$$\angle = \tan^{-1} \left( \frac{X_C}{R} \right)$$

$$v = V_m \sin \omega t$$

$$i = I_m \sin(\omega t + \phi)$$

Power

$$P = V \cdot I$$


$$= V_m \sin \omega t \cdot I_m \sin(\omega t + \phi)$$

$$= \frac{V_m I_m}{2} [\cos \phi - \cos(2\omega t + \phi)]$$


Average Power


$$P_{avg} = \frac{V_m I_m}{2} \cos \phi$$

$$P_{avg} = VI \cos \phi$$

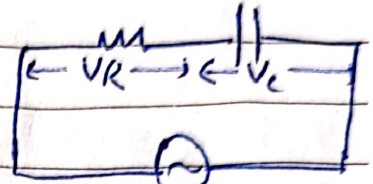


$$v = V_m \sin \omega t$$

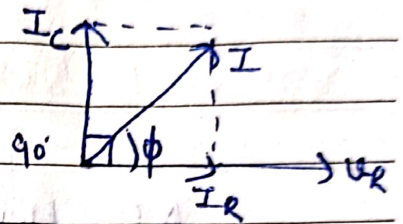

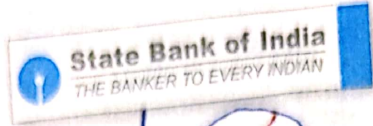


JUNE 2014						
M	T	W	T	F	S	S
30	1	2	3	4	5	6
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

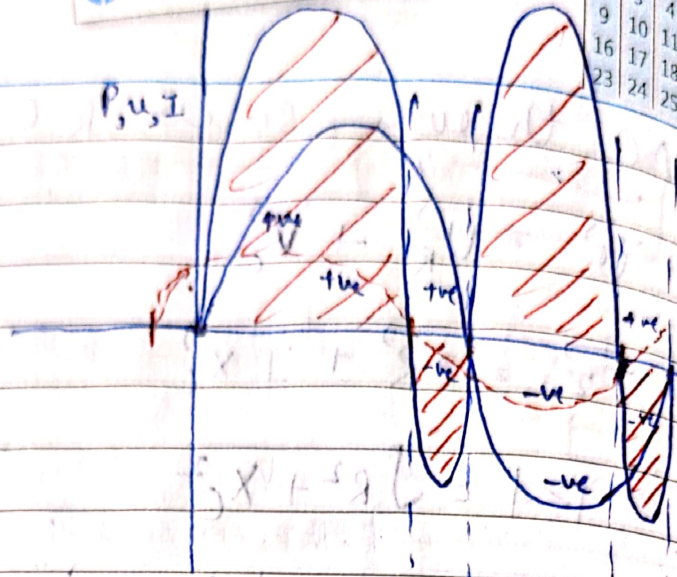

AC through series RLC circuit

$$Z = R + jX_L - jX_C$$


$$= R + j(X_L - X_C)$$

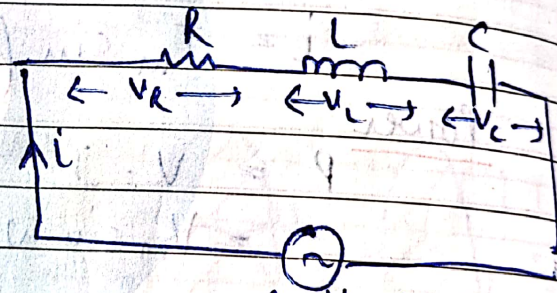

① When  $X_L$  is greater than  $X_C$   
 $X_L > X_C$

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$
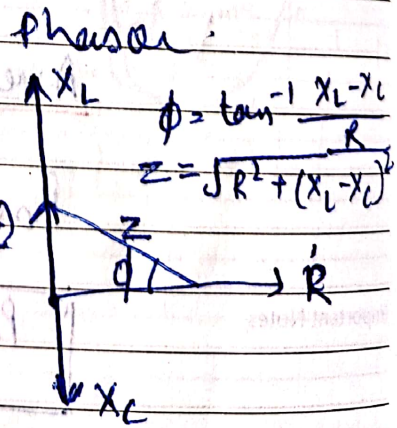
$$\phi = \tan^{-1} \frac{(X_L - X_C)}{R}$$



Important Notes

Circuit will be inductive

because  $X_L$  is greater as compared to  $X_C$




JUNE 2014						
M	T	W	T	F	S	S
30						
2	3	4	5	6	7	8
9	10	11	12	13	14	15
16	17	18	19	20	21	22
23	24	25	26	27	28	29

## Concept of Power

Apparant Power :- Apparant


power (S) is product of rms value of Voltage (V) & current (I).

$$S = VI \quad \text{Unit KVA}$$

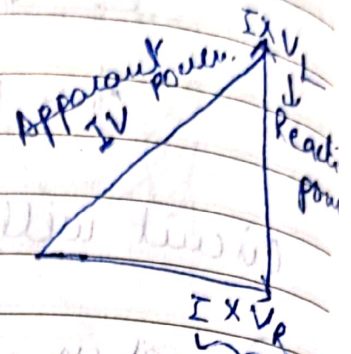

Active / True Power or Real power :-

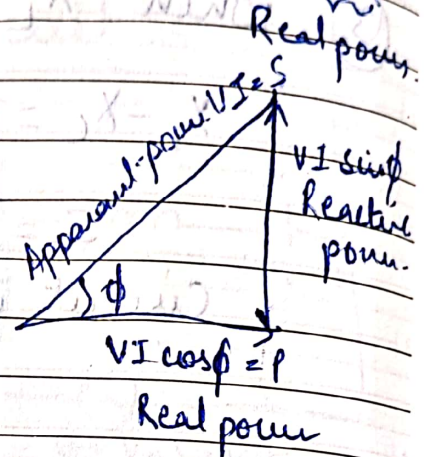True Power (P) is product of applied Voltage (V) and active component of current (I).



$$P = VI \cos \phi = S \cos \phi \quad \text{Unit - KW}$$

Reactive Power :-

Reactive Power (Q) is product of applied voltage (V) & reactive component of current (I)

$$Q = VI \sin \phi = S \sin \phi \quad \text{unit = KVAR}$$

JULY 2014						
1	2	3	4	5	6	
7	8	9	10	11	12	13
14	15	16	17	18	19	20
21	22	23	24	25	26	27
28	29	30	31			

## Power factor

- Power factor is ratio b/w true power & apparent power.
- Ratio of resistance to Impedance.
- cosine of phase angle b/w Voltage & current

## Cause of low Power factor

- All AC motor transformers has low power factor.
- Most of the loads has low power factors.
- Industrial heating furnace, induction furnace has low power factor.

## Improvement of power factor

- Using Phase advancers.
- Using Capacitor Bank, Synchronous Condensers.

Important Notes


## Effects of low p.f.

- large copper losses b) large KVA rating c) Poor Voltage Regulation.

Numericals of series

Q A 120 V, 60 W lamp is to be operated on 220V, 50 Hz supply mains. In order that lamp should operate on correct voltage. Calculate value of (i) Non Inductive resistance, (ii) Pure inductance (iii) Pure capacitance.

Lamp is also resistive.

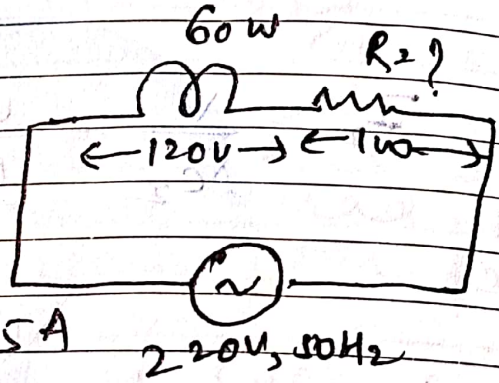

Sol: (i) Lamp \$P = 60W\$, \$U = 120V\$

$$i = \frac{P}{U} = \frac{60}{120} = 0.5A$$

The value of R


$$R = \frac{V}{I} = \frac{100}{0.5} = 200\Omega$$

(ii) 
$$V = \vec{V}_R + \vec{V}_L$$

$$V_L = \sqrt{V^2 - V_R^2}$$

$$= \sqrt{220^2 - 120^2}$$

$$= 184.89V$$

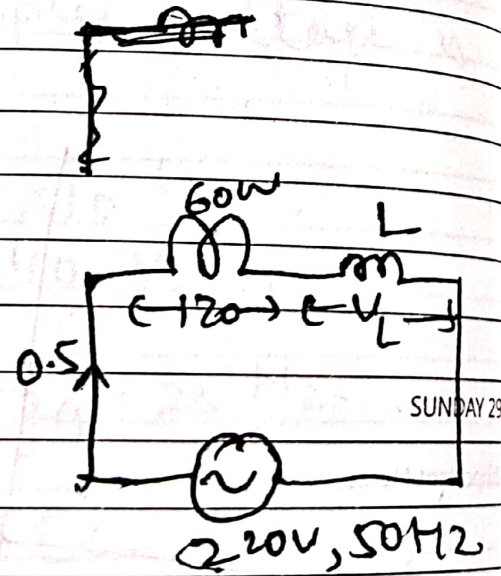

Important Notes

